

# lecture 6

## Sequential circuits 2

- T flipflops, counters and timers (finishing last lecture)
- register array
- RAM


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

January 27, 2016


# TODAY: from flip flops to RAM

 


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

# T flip flop (toggle)

 


Assume falling edge triggered.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

Q: What does this circuit do ?

Assume falling edge triggered flip flops.


$Q_i$  is the clock input for flip flop  $i + 1$ .



Assignment Project Exam Help

$i$  increases from left to right.

<https://powcoder.com>

Add WeChat powcoder

 


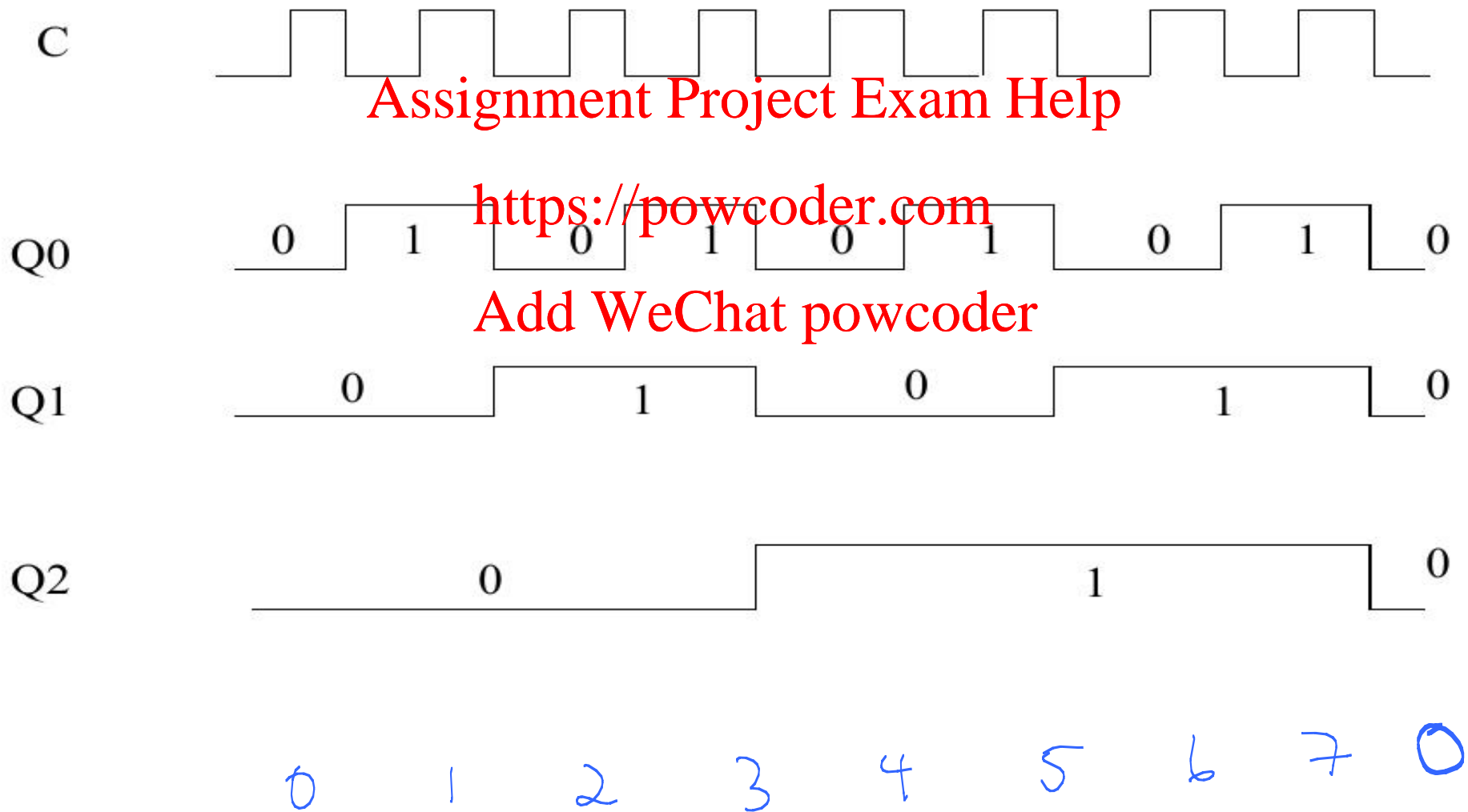 

Correction of incorrect claim made from last lecture (see below).

## D flip flop ("rising edge triggered")

Assignment Project Exam Help

 

By putting the inverter on the first D latch, we would make Q change its value on the rising edge of the clock. ~~There is no advantage to this, so for simplicity we will always work with falling edge triggered.~~


Assume **rising** edge triggered.


Q: What does the circuit do ?

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

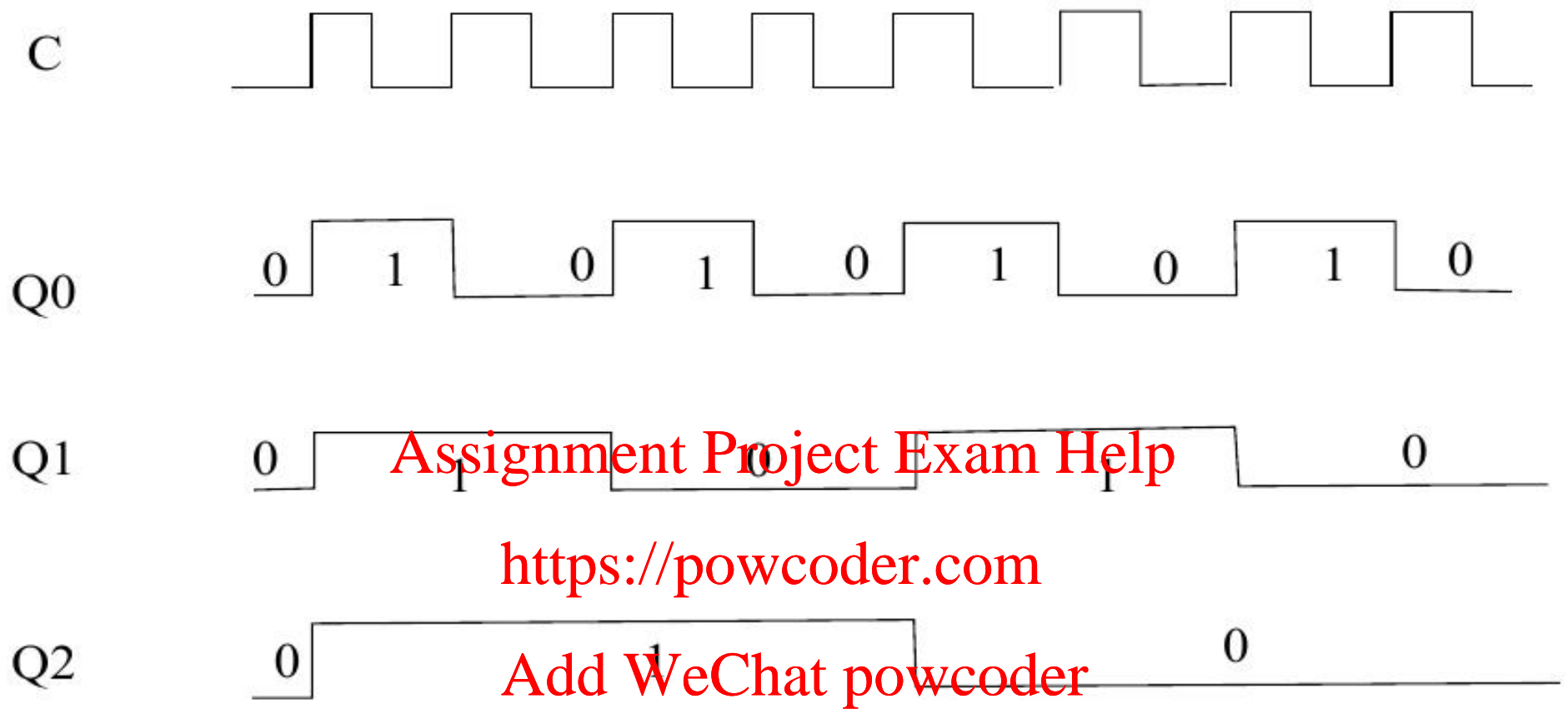

A: 0 7 6 5 4 3 2 1 0

Timer (count down)



# lecture 6

## Sequential circuits 2

- T flipflops, counters and timers
- register array [recall what a register is]  
<https://powcoder.com>
- RAM  
Add WeChat powcoder

January 27, 2016


# Register Array

register	0
register	1
register	2
Assignment Project Exam Help	
<a href="https://powcoder.com">https://powcoder.com</a>	
Add WeChat powcoder	
register	30
register	31

In MIPS, there are 32 registers, and each is 32 bits. There is no significance to the fact that the number of registers is the same as the number of bits per register.

$$x = y + z$$

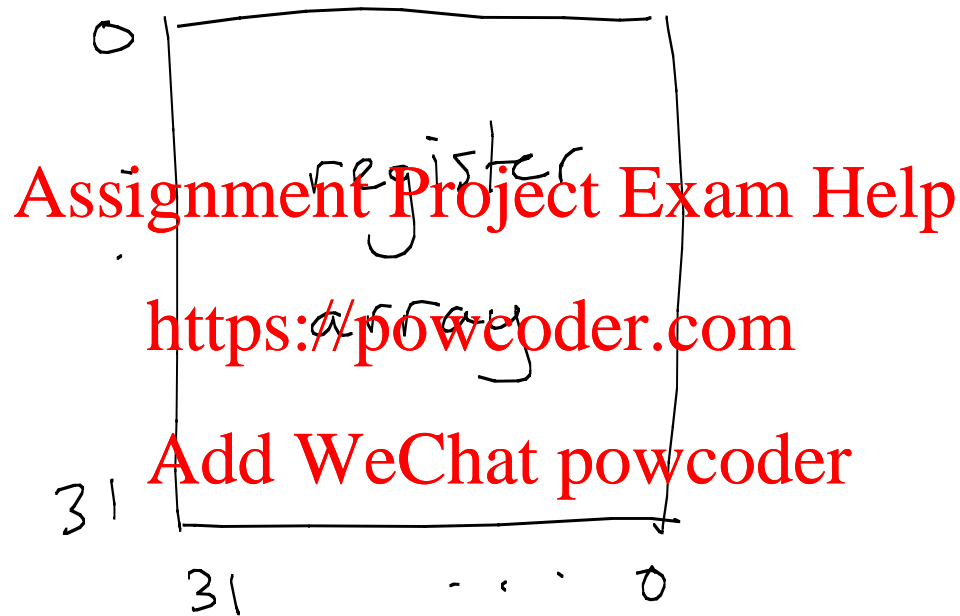Suppose the variables **x**, **y**, **z** are stored in registers.



How to read **y** and **z** ?


How to write the result into **x** ?

Recall idea from last lecture:


Use sets of D flip flops (register) to store numbers A and B.

Compute  $A + B$  using the circuit shown, and write the new value back into B. <https://powcoder.com>

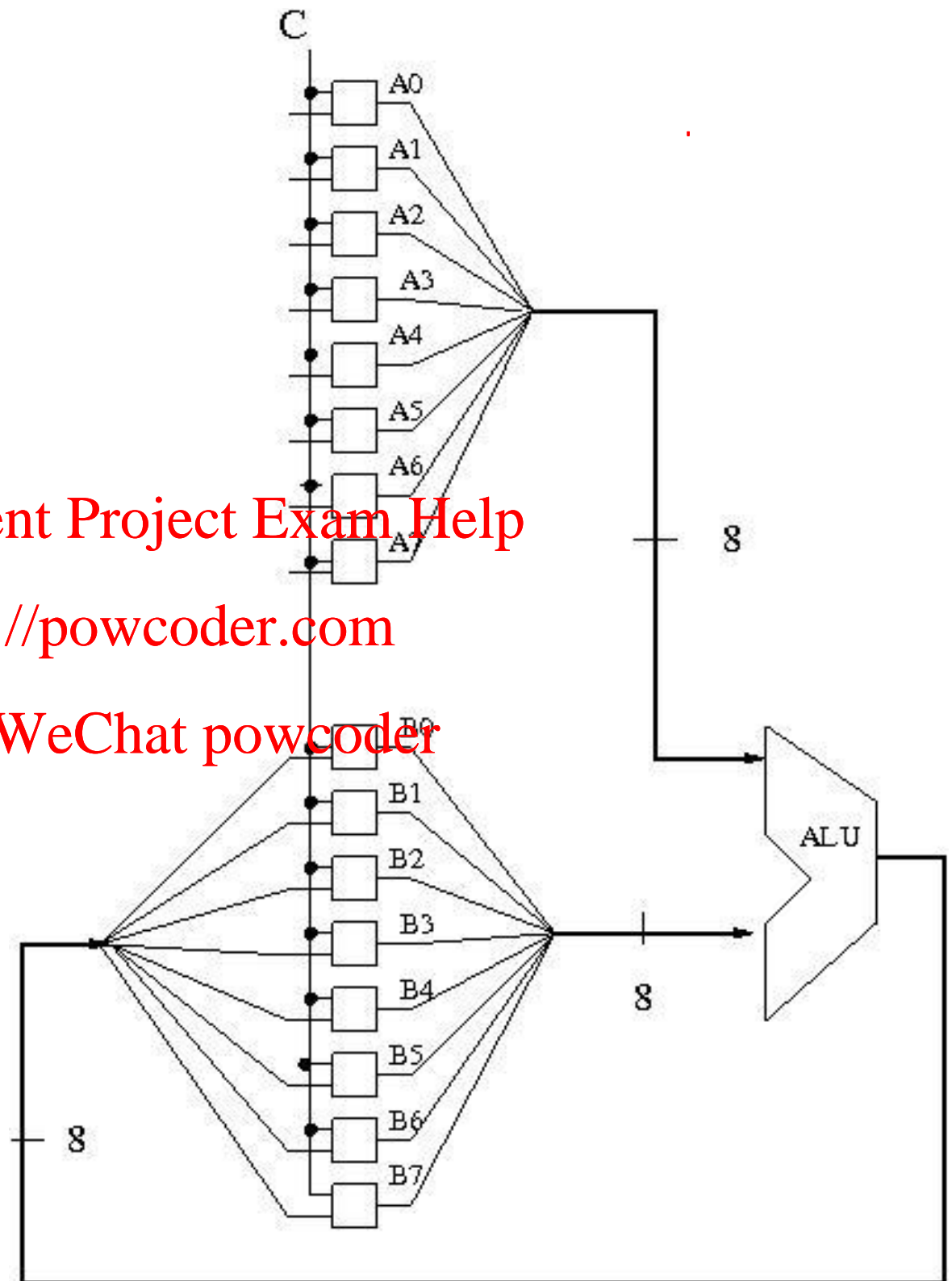For the next slide, we will rotate A and B so they are horizontal oriented and have 32 of them (not 2), each 32 bits (not 8).



# ReadReg

 


There are  $32 \times 32 = 1024$  data wires fed into the multiplexor. In fact, there are 32 separate 1 bit multiplexors, each using the same 5 bit selector code.

$$x = y + z$$

ReadReg1

specify which register is y

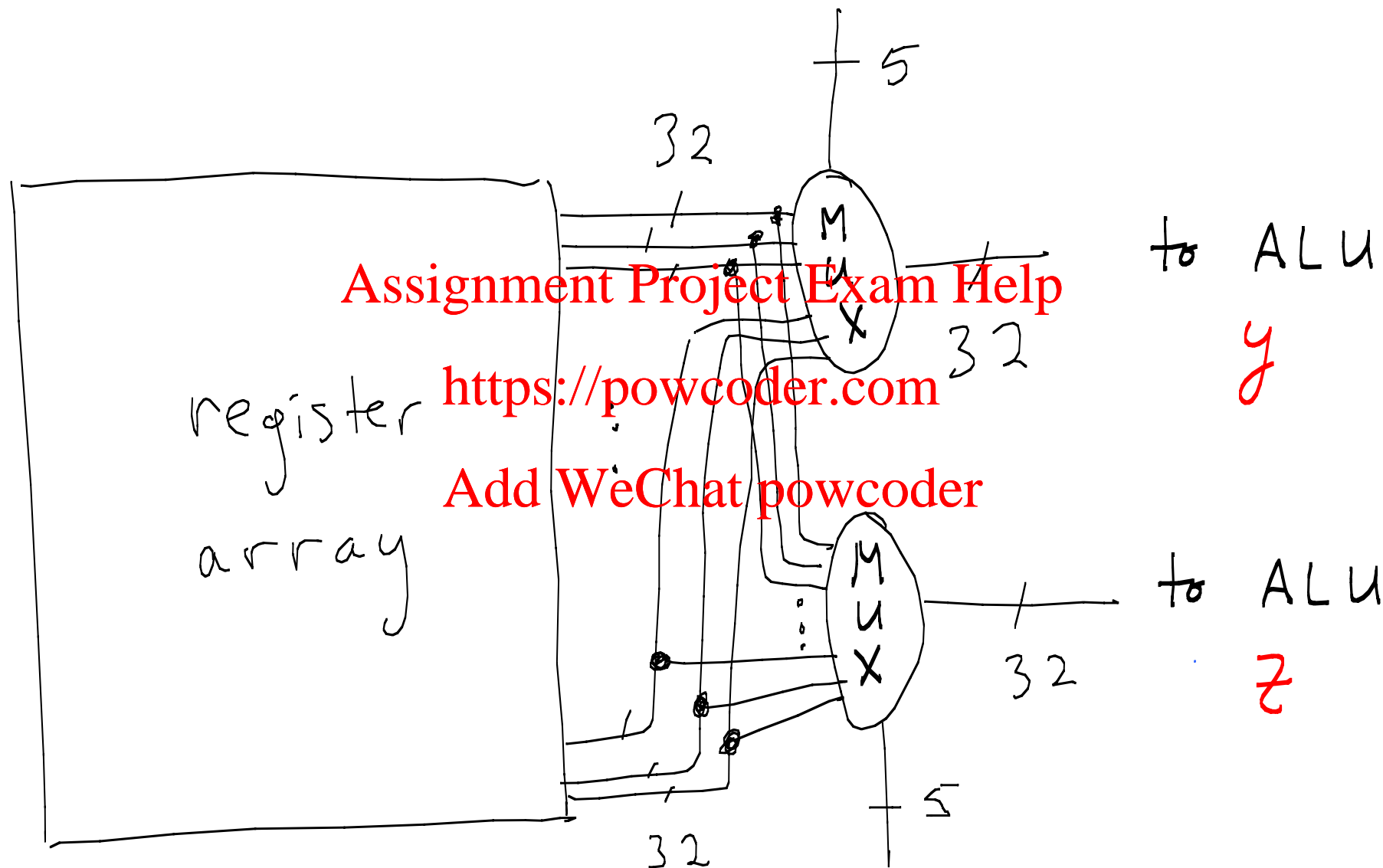


ReadReg2

specify which register is z

$$x = y + z$$

WriteEnable

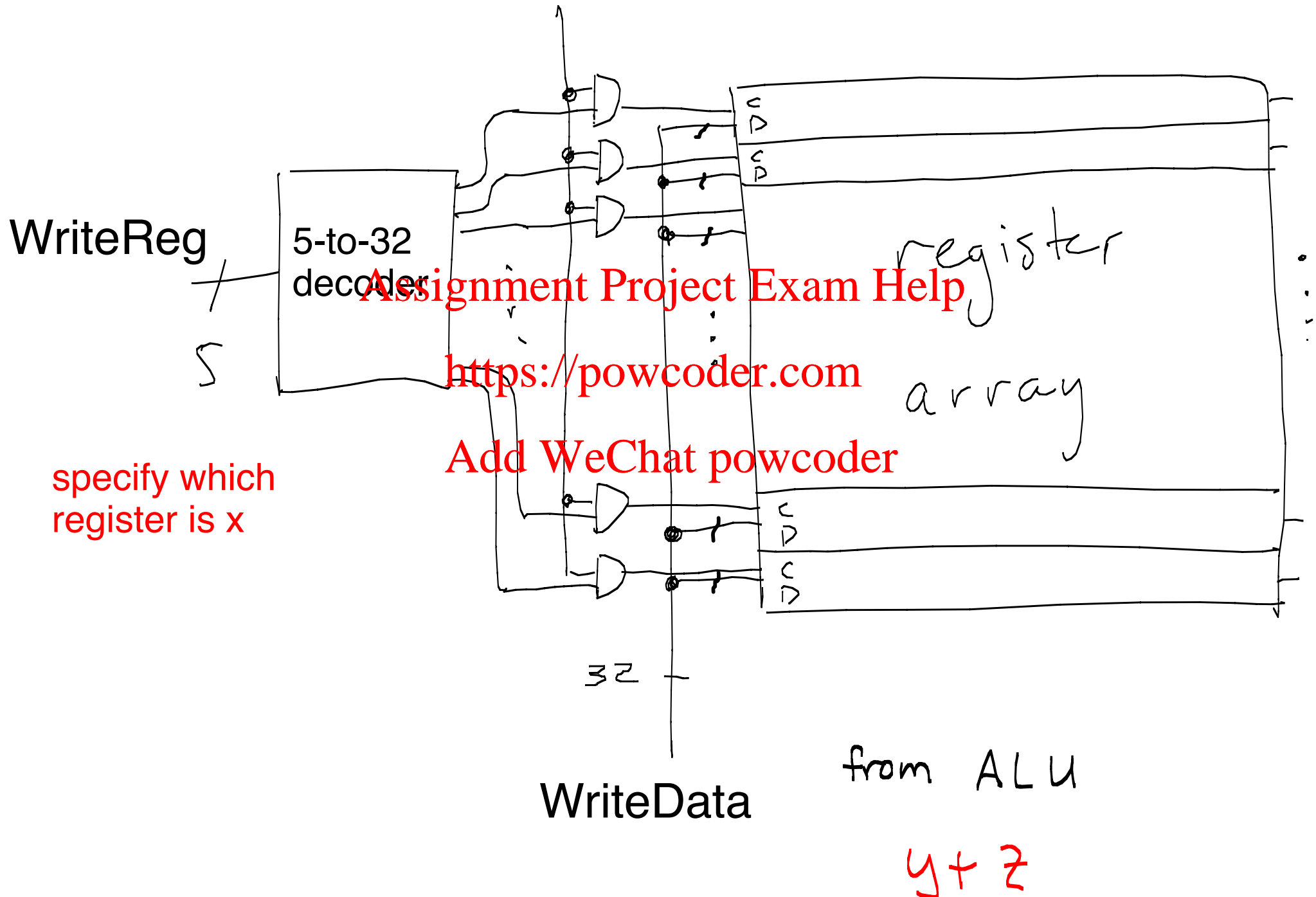

[ADDED SLIDE]

I neglected to mention in the lecture that the clock signal C is embedded in the WriteEnable signal. That is, WriteEnable = 1 if the clock C is 1. Note this is not an "if or only if", rather

Assignment Project Exam Help

WriteEnable = AND(C, we)


<https://powcoder.com>

I won't write the clock explicitly in the future since it is understood that when we are working with registers, we always need a clock to synchronize the writes.


Add WeChat powcoder



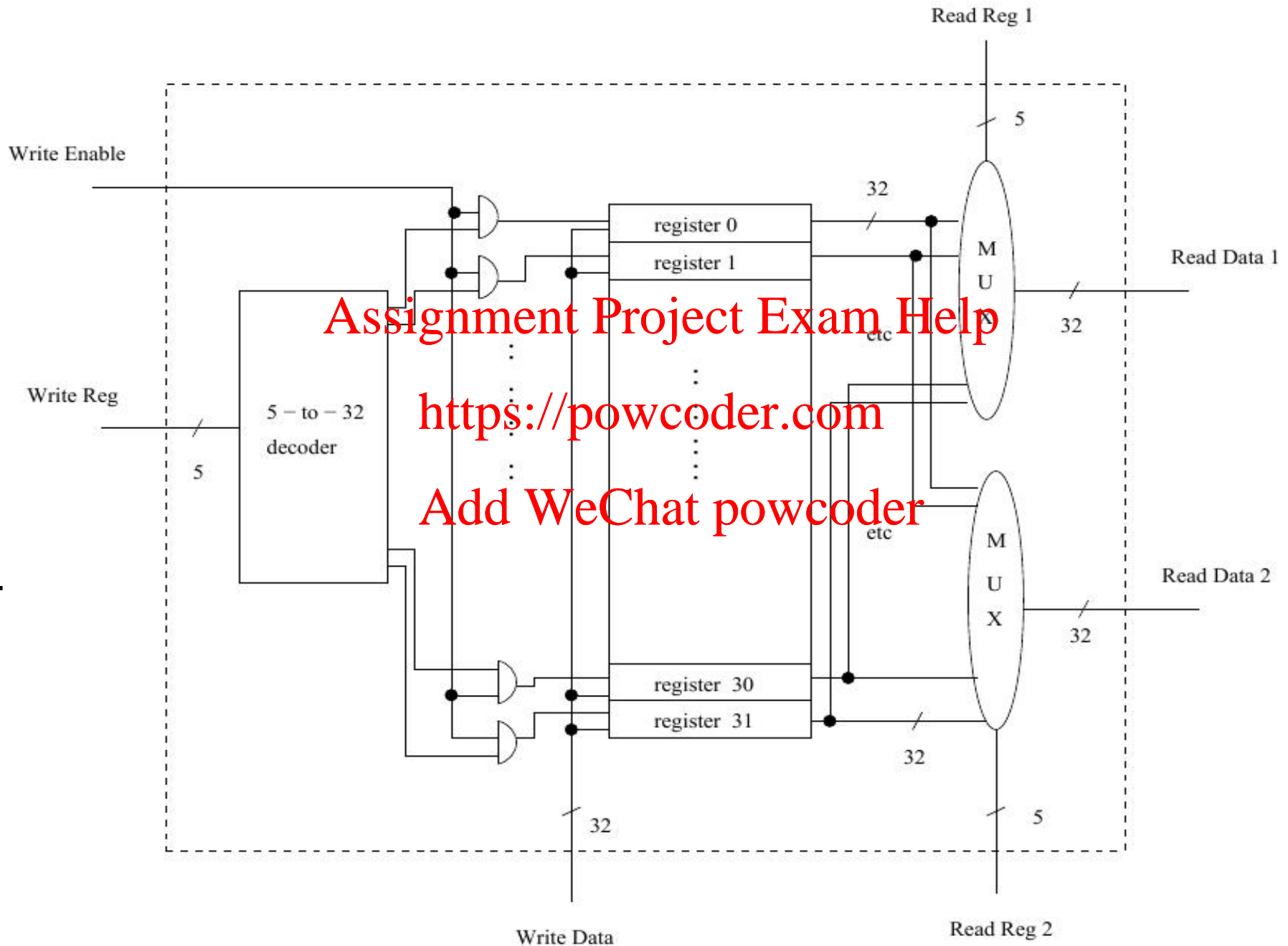... putting those last two slides together....



 Sometimes we write as follows (inputs on left, outputs on right).



WriteEnable


ReadReg1

ReadReg2

WriteReg

WriteData

operation

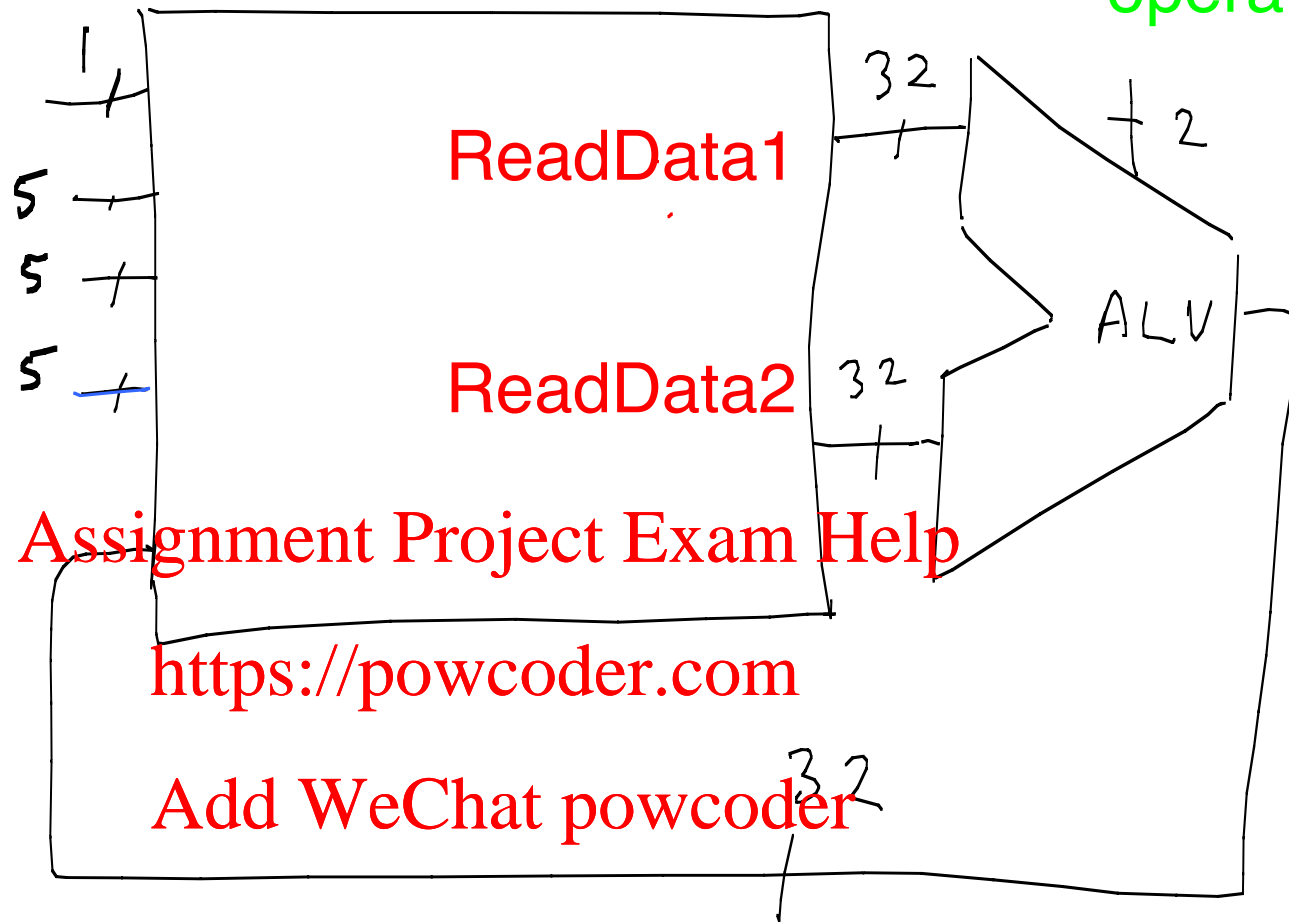


address

data


control

types of signals

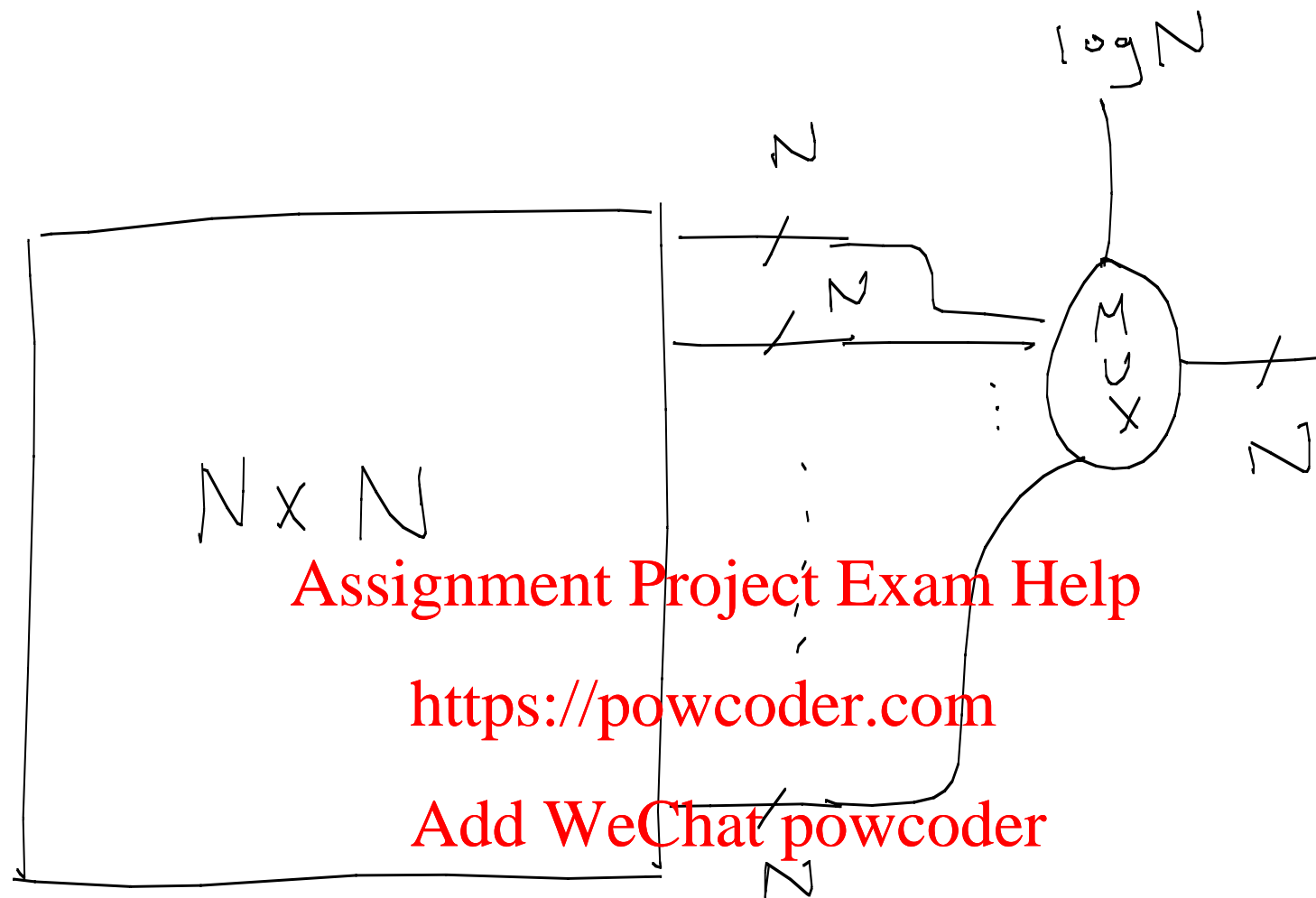

For larger memory arrays, the multiplexor design is not physically feasible. You need  $N^2$  wires coming out. But the side of the square array only grows with  $N$ .

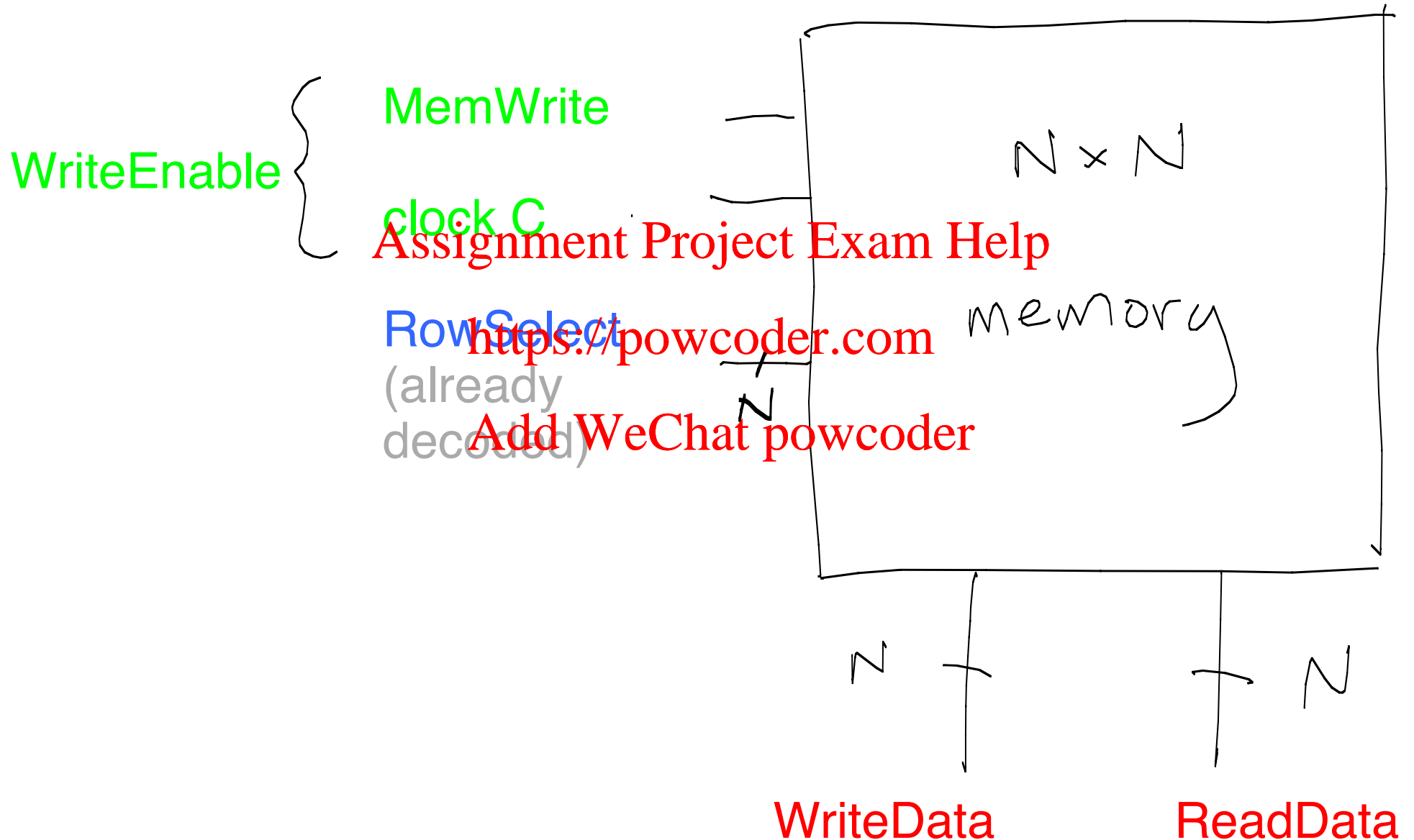An alternative approach ? .... somehow have only  $2N$  wires, namely a read and a write wire for each column.



Consider what happens for each of the  $N^2$  flip flops.  
All flip flops in a row (column) share the same horizontal (vertical) wire.


MemWrite  
clock C  
RowSelect

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

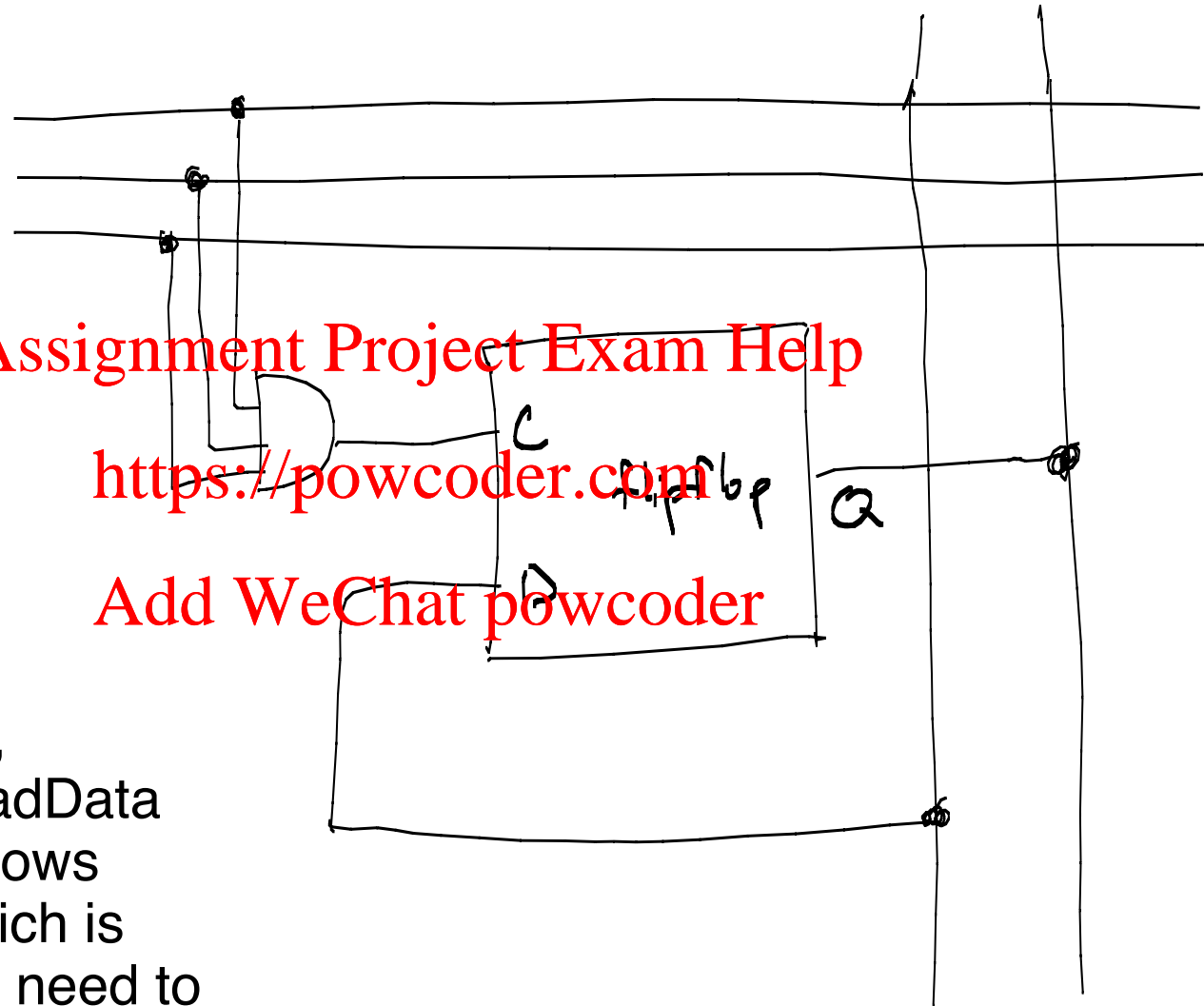There is a problem,  
however. The ReadData  
line reads from all rows  
simultaneously, which is  
not allowed. We need to  
select one. How ?





WriteData


ReadData
 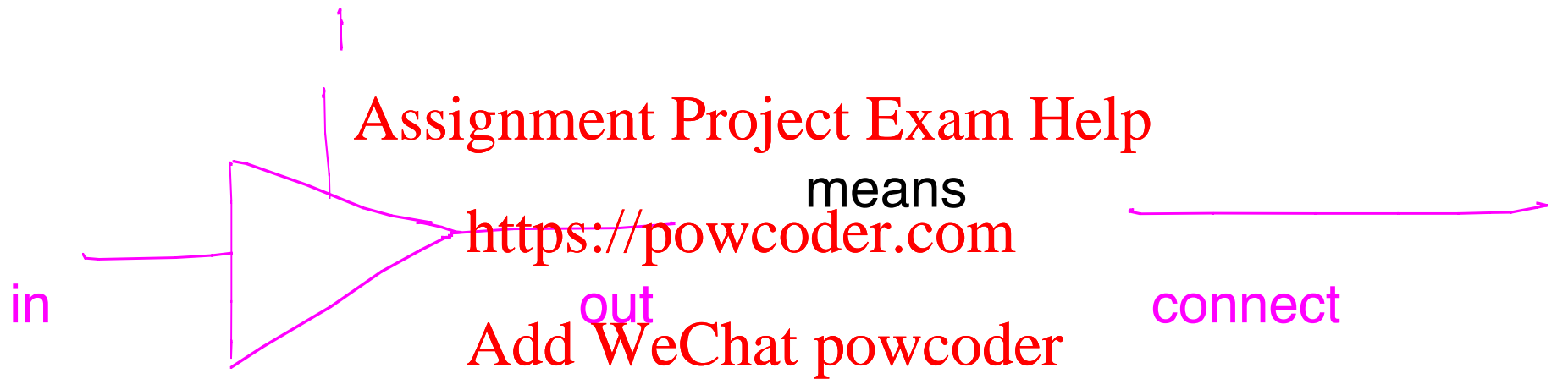
# Tri-state Gate (not a logic gate)

- also known as a 'tri-state buffer'
- output can have values 0, 1, or none  
(voltages are low, high, or zero)



RowSelect  
MemWrite  
clock C

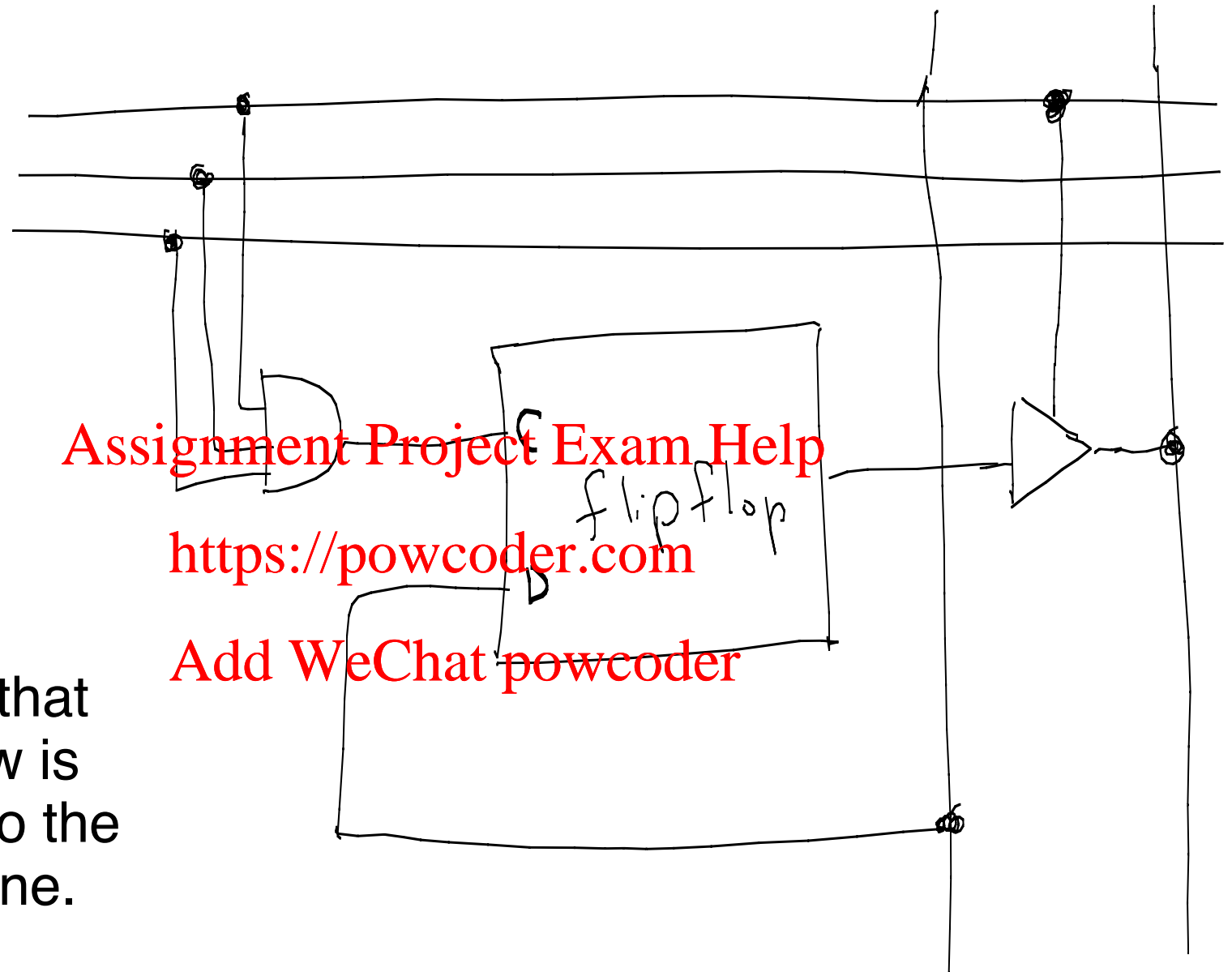

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


The idea is that  
only one row is  
connected to the  
ReadData line.

WriteData

ReadData



RowSelect  
MemRead  
MemWrite  
clock C

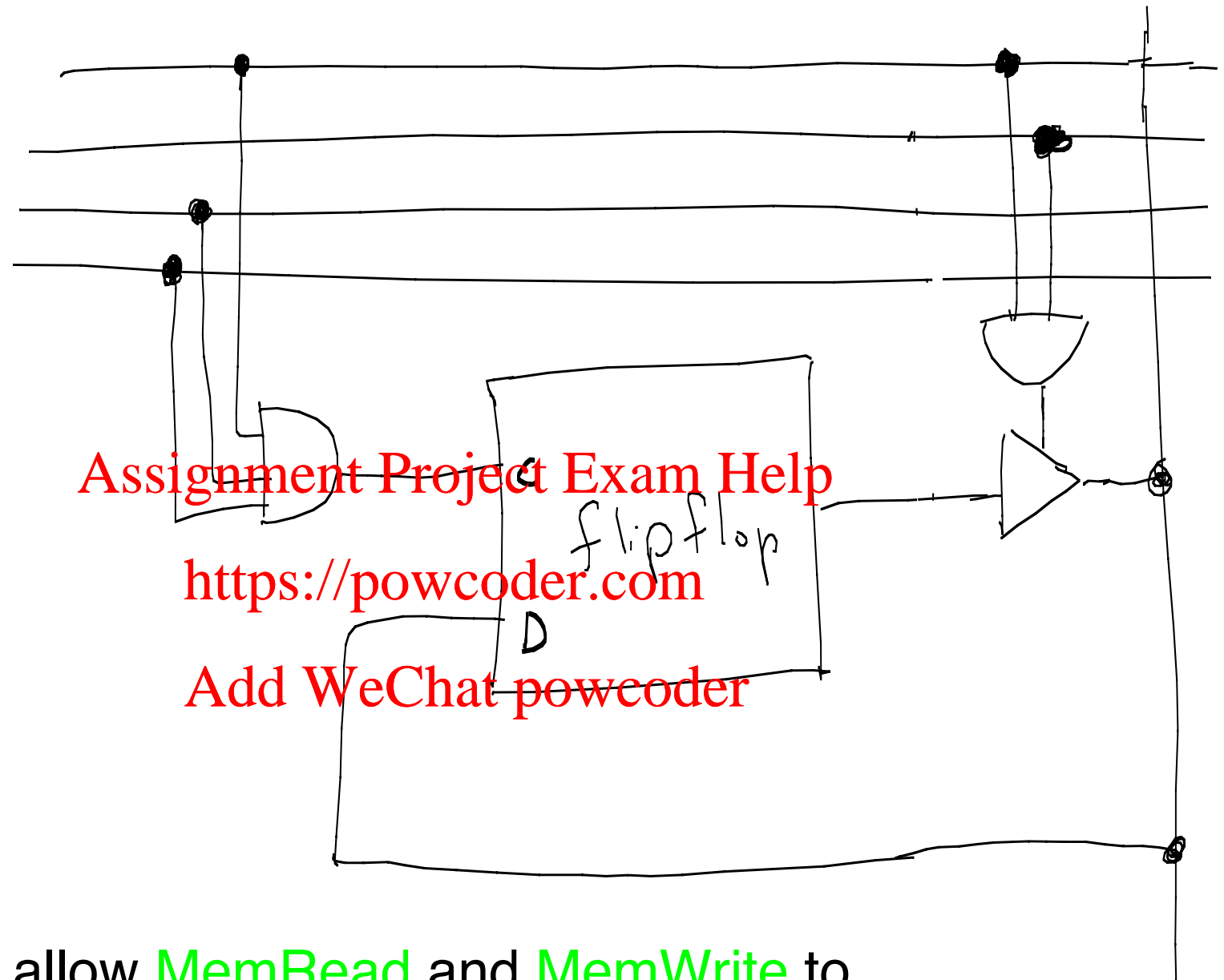

We would not allow MemRead and MemWrite to both be 1 (not shown in circuit). Also, sometimes neither would be 1.

Data

We have been thinking of reading or writing an entire row.

MemWrite

MemRead

clock C

RowSelect

(already decoded)


Assignment Project Exam Help

memory

<https://powcoder.com>


Add WeChat powcoder

Data

 

Let's next select only a single row and column.

RowSelect  
MemRead  
MemWrite  
clock C

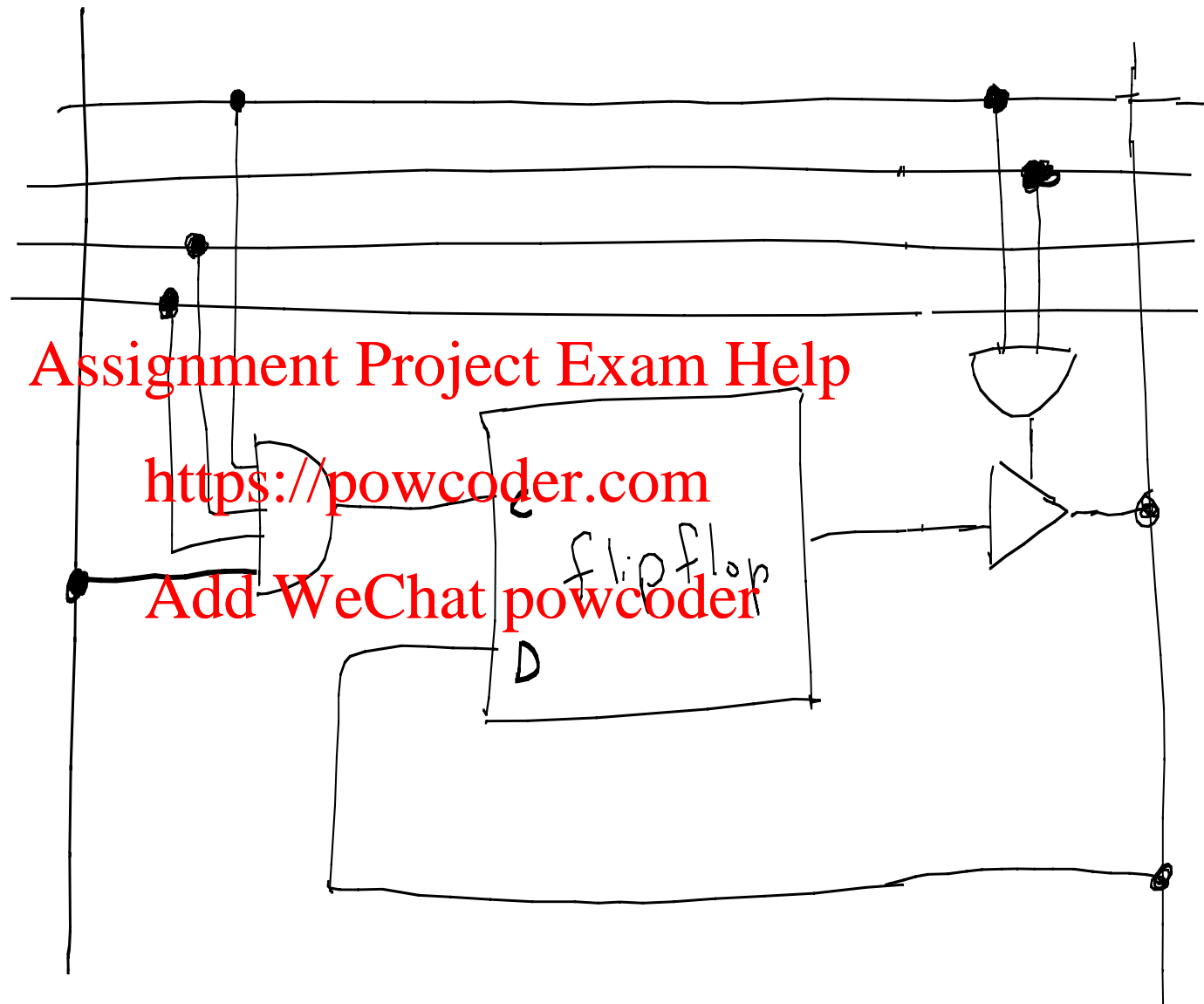

ColumnSelect

Data

1 bytes = 8 bits

1 KB =  $2^{10}$  bytes ("kilo")

1 MB =  $2^{20}$  bytes ("mega")

1 GB =  $2^{30}$  bytes ("giga")

1 TB =  $2^{40}$  bytes ("tera")

1 PB =  $2^{50}$  bytes ("peta")

1 EB =  $2^{60}$  bytes ("exa")

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

} RAM


e.g. Consider 8 chips with  $2^{16} \times 2^{15}$  bits on each chip.

This defines  $2^{31}$  bits per chip  
or  $2^{31}$  bytes (2 GB).

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

 

MemRead  
MemWrite  
clock C

$A_{30} \dots A_{15}$

 

16

2<sup>16</sup>


RowSelect

ColumnSelect

<https://powcoder.com>

Add WeChat poweoder

$A_{14} \dots A_0$

 

15

2<sup>15</sup>

Data