

# lecture 4

## Combinational logic 2

- ROM

Assignment Project Exam Help


- arithmetic circuits <https://powcoder.com>

Add WeChat powcoder

- arithmetic logic unit (ALU)

January 20, 2016

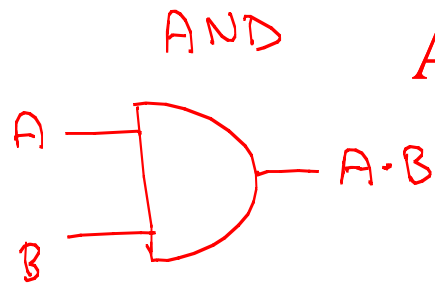
Last lecture: truth tables, logic gates & circuits




Assignment Project Exam Help  
<https://powcoder.com>

Add WeChat powcoder


OR

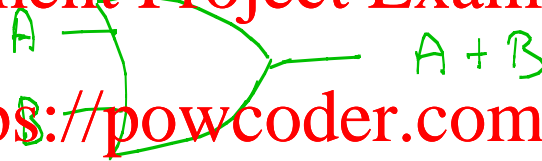


NOT

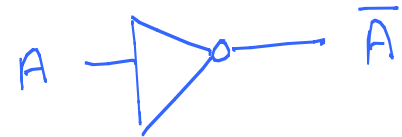


NAND

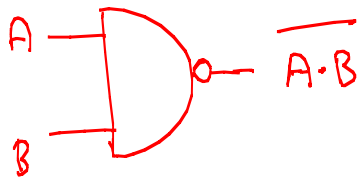

NOR

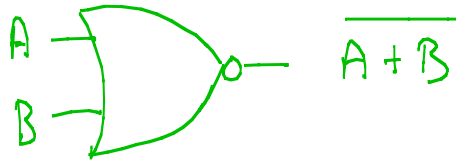


XOR

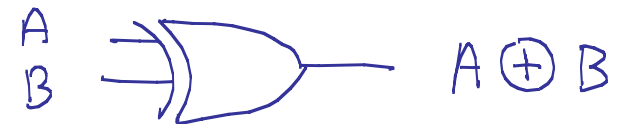

# Recall multiplexor (selector)

$$Y = \overline{S} \cdot A + S \cdot B$$

Assignment Project Exam Help

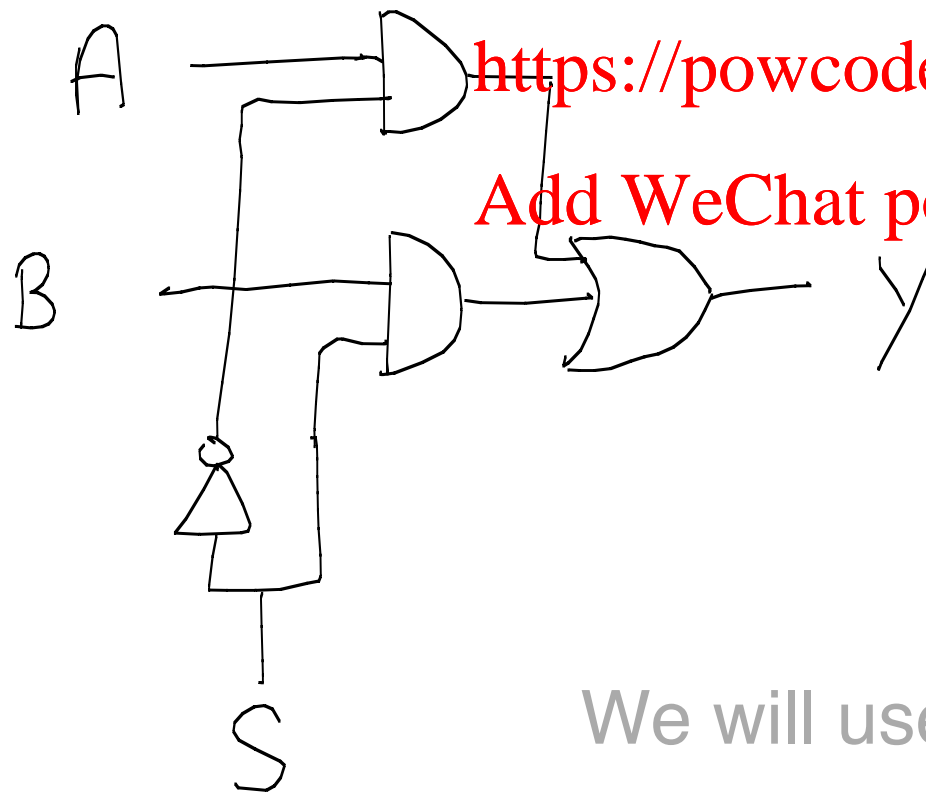

if S  
Y = B  
else  
Y = A

We will use this several times later.

# "Read-only Memory"

(leftover topic from last lecture)

$A_1$	$A_0$	$Y_2$	$Y_1$	$Y_0$
0	0	0	1	1
0	1	0	0	1
1	0	0	0	0
1	1	1	0	0

Sometimes we can think of a circuit as a "hardwired" memory (read only).

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

Note: the order of the  $A_1$   $A_0$  variables matters.

address      data

$A_1 A_0$

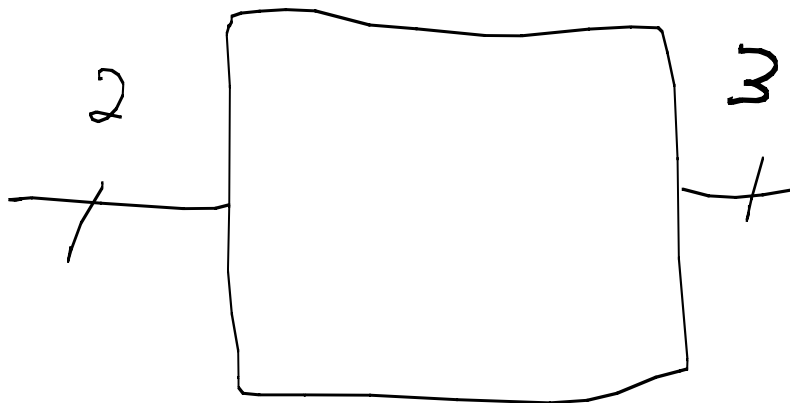

$Y_2 Y_1 Y_0$

# Recall: binary arithmetic

$$\begin{array}{r} C_{n-1} \dots C_2 C_1 C_0 \\ A_{n-1} \dots A_2 A_1 A_0 \\ + B_{n-1} \dots B_2 B_1 B_0 \\ \hline S_{n-1} \dots S_2 S_1 S_0 \end{array}$$

Assignment Project Exam Help  
<https://powcoder.com>  
Add WeChat powcoder

Notes:

- $C_0 = 0$
- $A, B$  could represent signed or unsigned numbers

Let's build an "adder" circuit.

$$\begin{array}{r}
 C_{n-1} \dots C_2 C_1 \\
 A_{n-1} \dots A_2 A_1 A_0 \\
 B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

$A_0 B_0$		$S_0$	$C_1$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S_0 =$$

$$C_1 =$$

# Half Adder


$$S = A \oplus B$$

$$C = A \cdot B$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

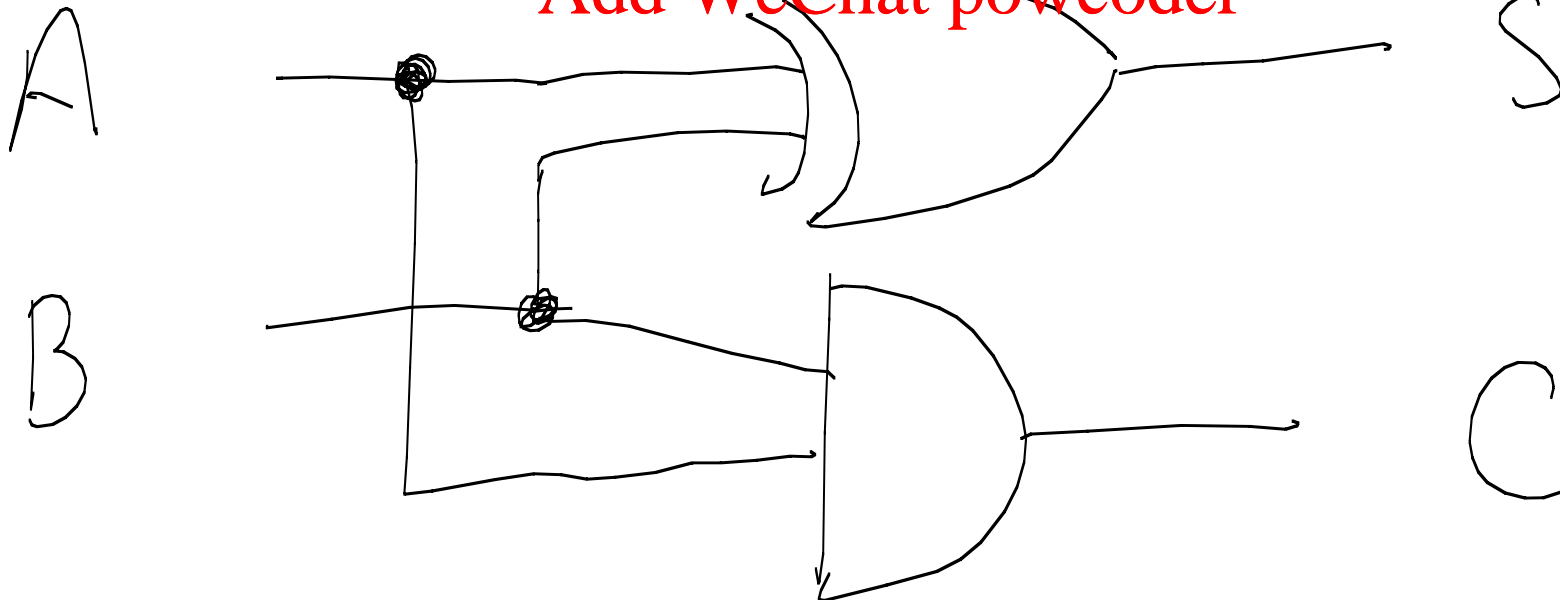

$C_{n-1} \dots C_2 C_1 C_0$

$A_{n-1} \dots A_2 A_1 A_0$

$B_{n-1} \dots B_2 B_1 B_0$

---


$S_{n-1} \dots S_2 S_1 S_0$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


full adder

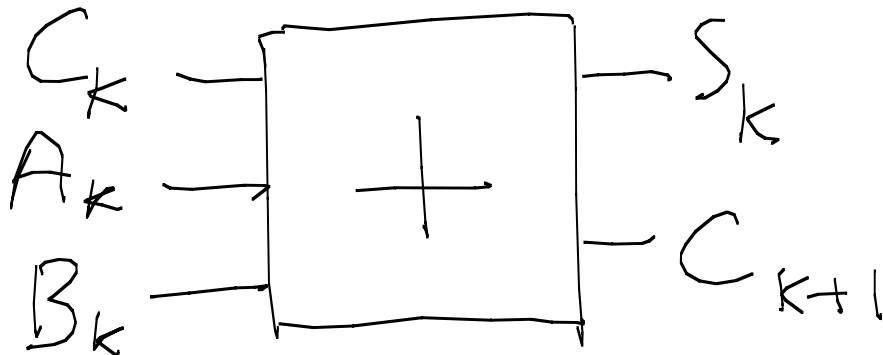

$A_k$	$B_k$	$C_k$	$S_k$	$C_{k+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Ripple Adder

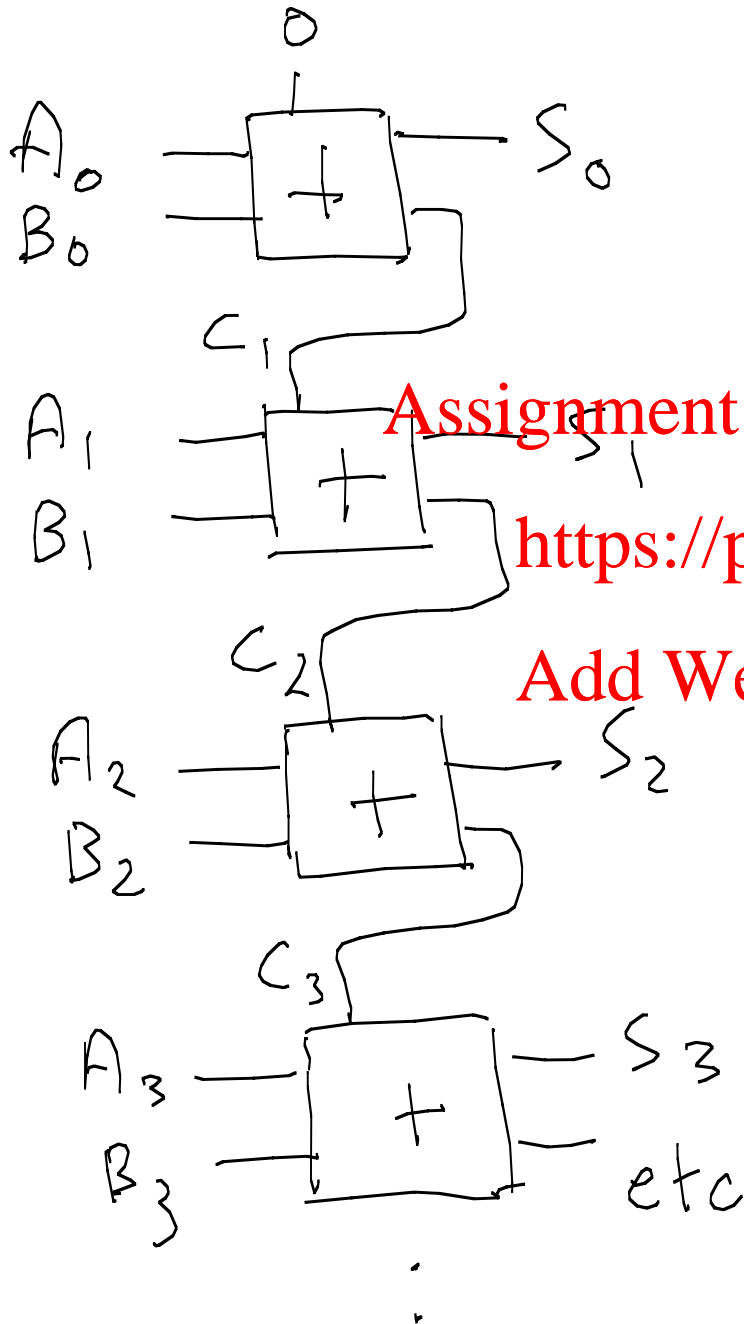

If  $n = 32$ , then we can have a long delay as carries propagate through the circuit. We'll return to this later.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

$$\begin{array}{r}
 C_{n-1} \dots C_2 C_1 C_0 \\
 A_{n-1} \dots A_2 A_1 A_0 \\
 + B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

As I mentioned before.... the *interpretation* of the S bit string depends on whether the A and B bit strings are signed or unsigned.

However, the full adder circuit does not depend on whether A and B are signed or unsigned.

# Overflow

We still might want to know if we have "overflowed" :

e.g. - if the sum of two positive numbers yields a negative


- if the sum of two negative numbers yields a positive

**Assignment Project Exam Help**

How can we detect these two cases ? (see Exercises 2)

<https://powcoder.com>


**Add WeChat powcoder**

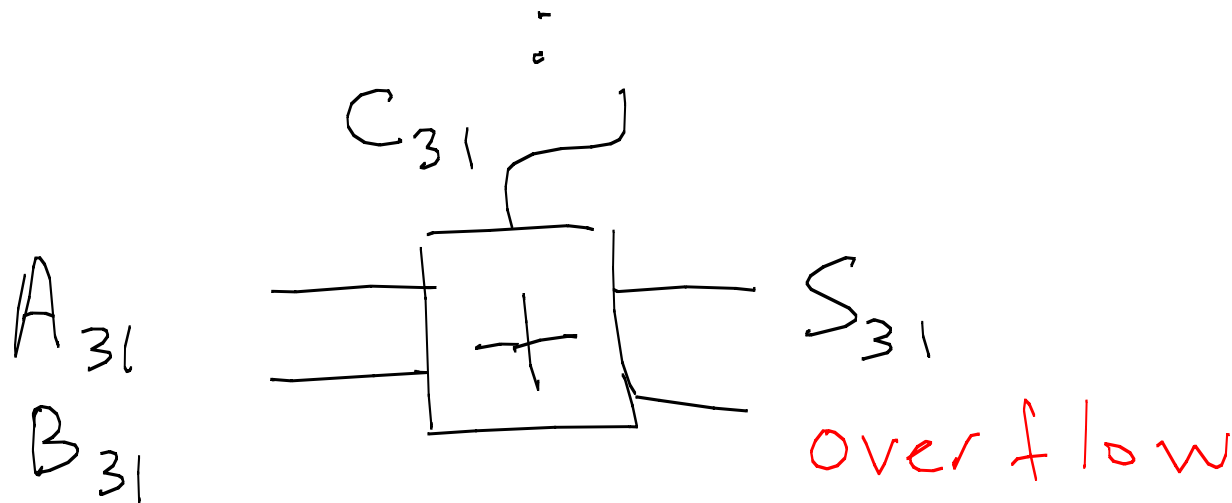

# TODO TODAY

- encoder
  - decoder
  - n-bit multiplexor
  - fast adder
  - ALU
- Assignment Project Exam Help
- <https://powcoder.com>
- Add WeChat powcoder

# Encoder

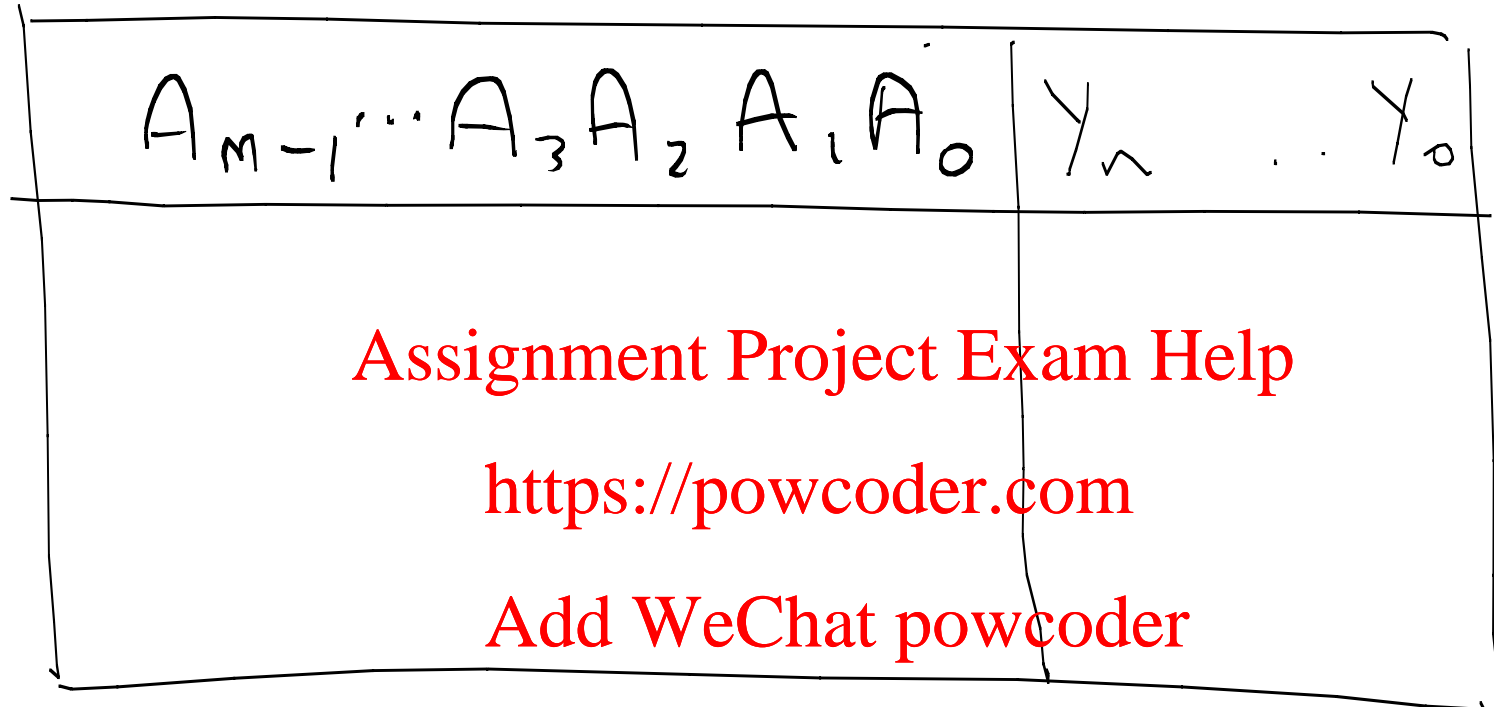

many bits

code  
(few bits)

# Encoder Example 1

panel with  
five buttons

$b_4$	$b_3$	$b_2$	$b_1$	$b_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	1	0	0	0	0	1	1
1	0	0	0	0	1	0	0

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

This assumes only one button can be pressed at any time.

panel with  
five buttons



$b_4$	$b_3$	$b_2$	$b_1$	$b_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	0
X	X	X	X	1	0	0	1
X	X	X	1	0	0	1	0
X	X	1	0	0	0	1	1
X	1	0	0	0	1	0	0
1	0	0	0	0	1	0	1

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

This allows two buttons to be pressed at the same time (and  
encodes the one with the highest index).

lowest

# Encoder Example 2



panel with  
ten buttons

6 9 0 0 0 0

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

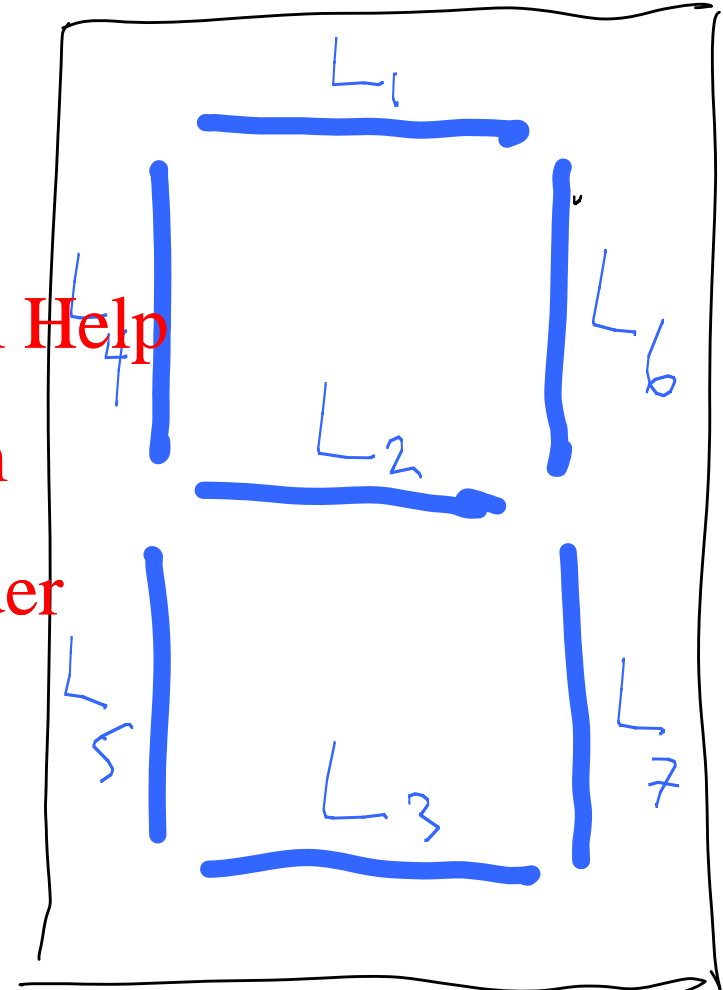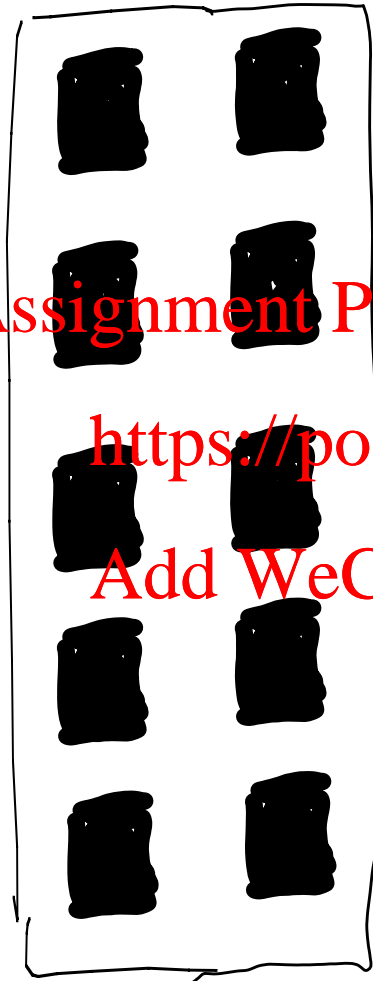

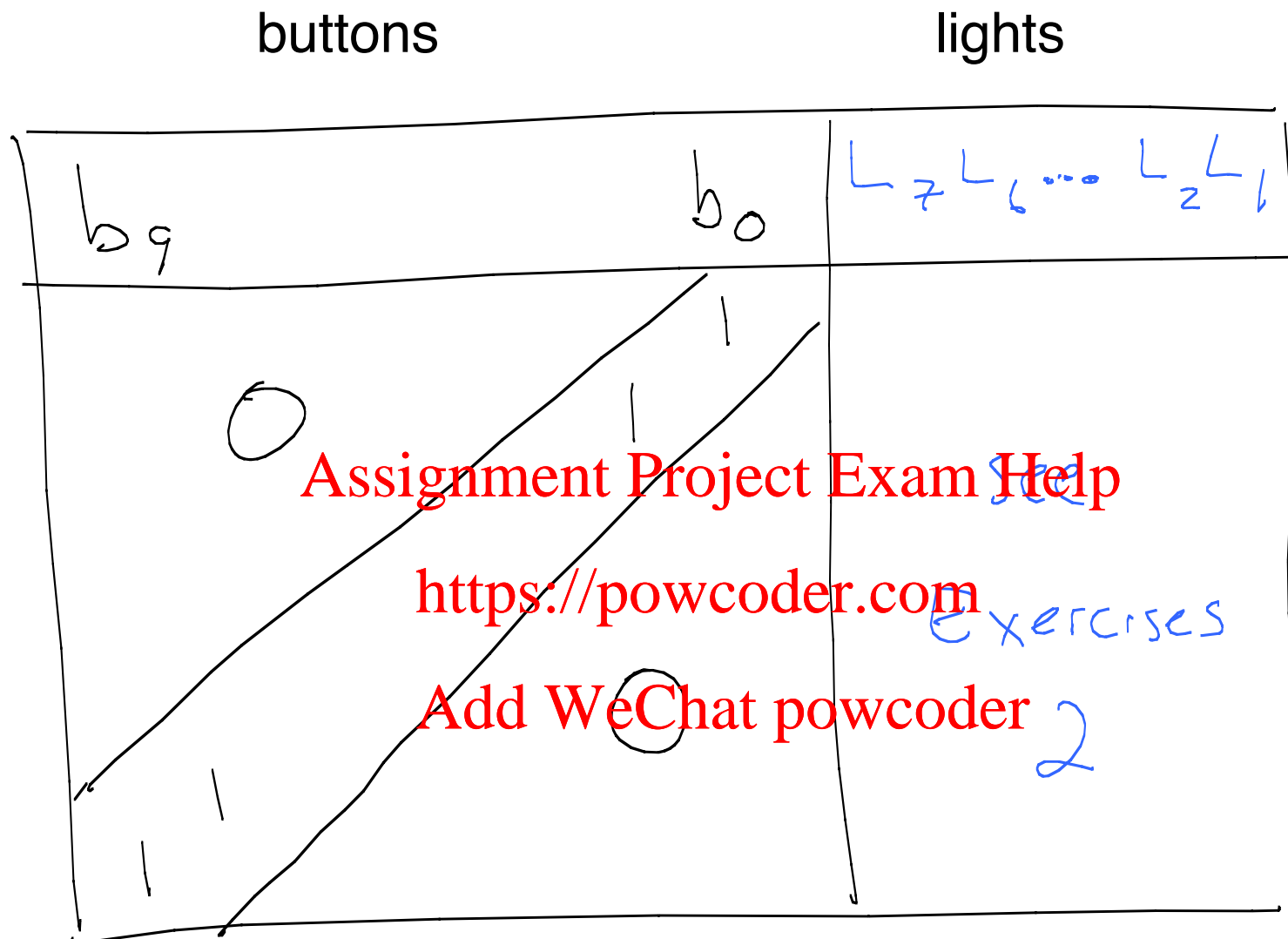display e.g. on a  
digital watch,  
calculator, etc.





Each light  $L_i$  is turned on (1) by some set of button presses.

Each button  $b_k$  turns on (1) some set of lights.


# Decoder

$b_2$	$b_1$	$b_0$	$y_7$	$\dots$	$y_2$	$y_1$	$y_0$
0	0	0	1				
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

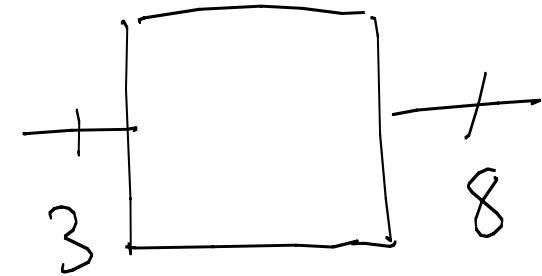

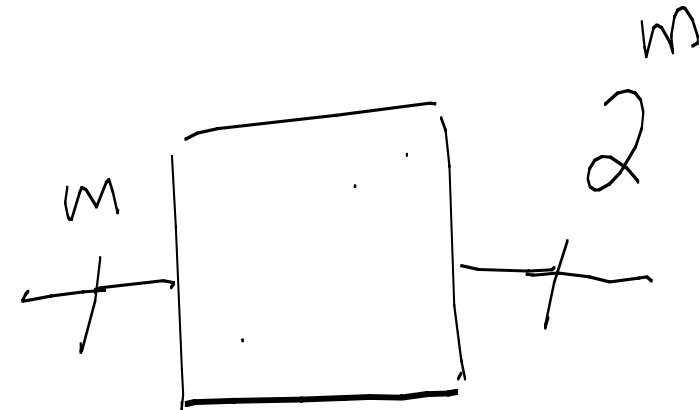
code word (in this example, it specifies which output is 1)


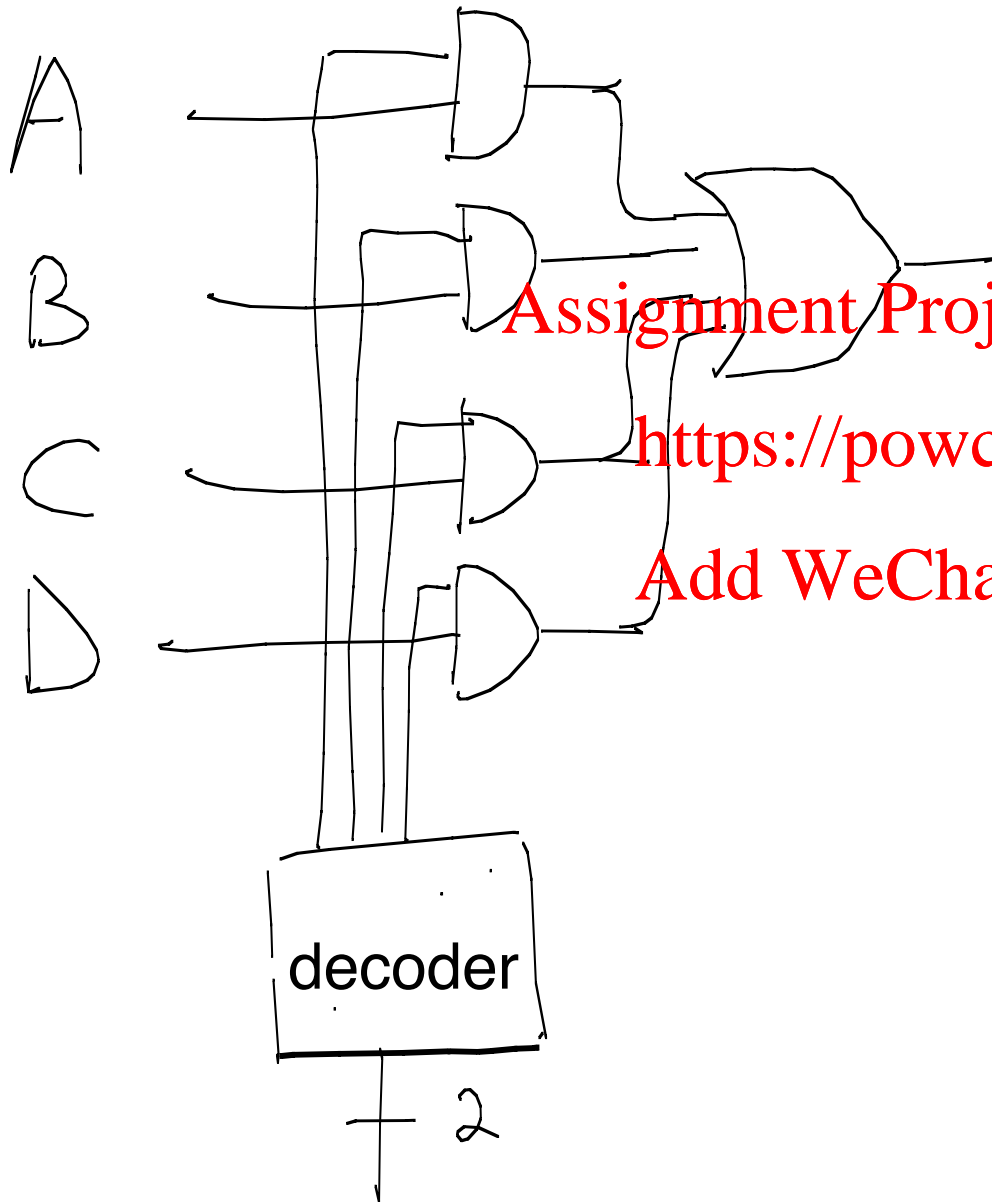
# 2-bit multiplexor

Also called a selector.

With 2 bits for the S you can select between  $2^2$  or 4 inputs.




Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

Notation:

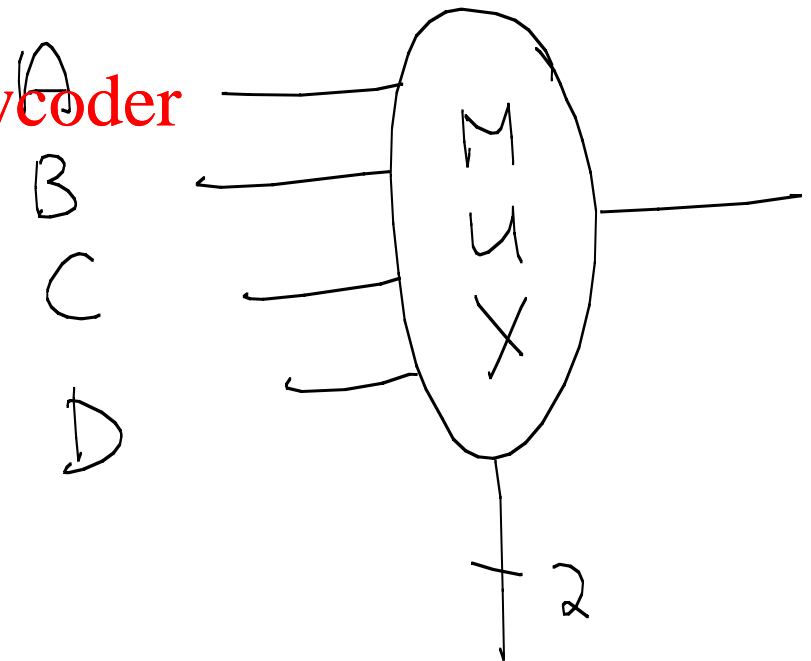
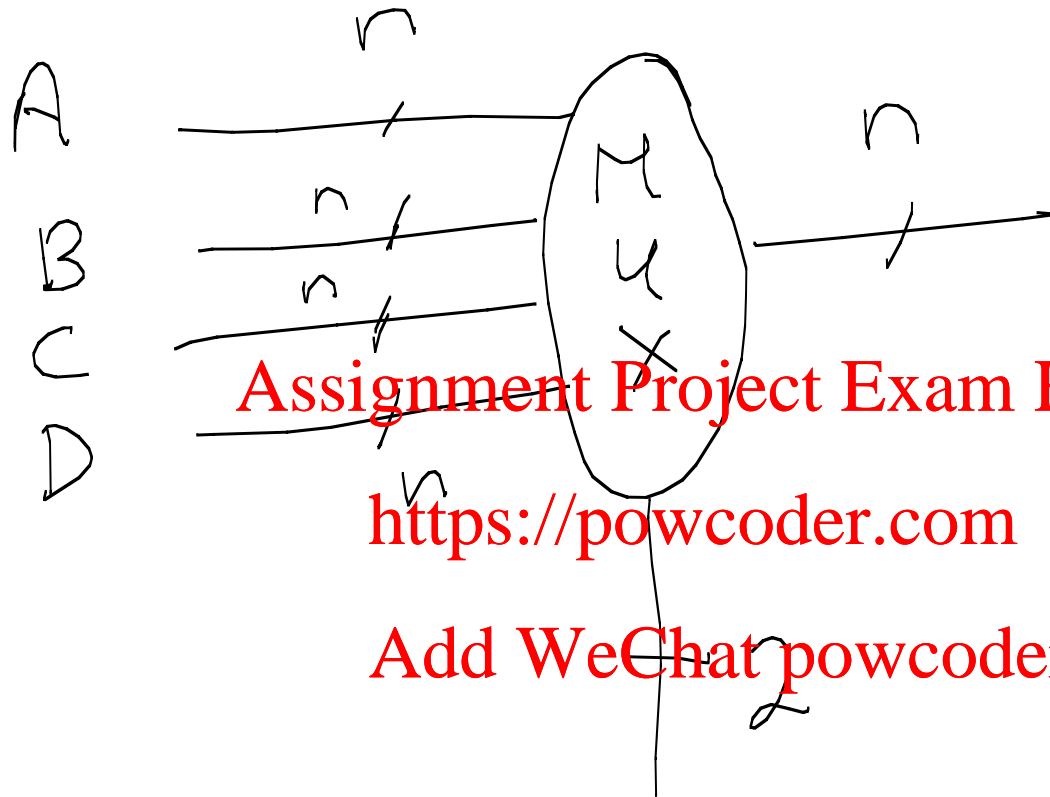
# More general example (2-bit multiplexor)




Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Selects from four  $n$ -bit inputs. For each  $A_i$ ,  $B_i$ ,  $C_i$ ,  $D_i$ , we replicate the circuit on the previous slide, but use the same decoder circuit.

# n-bit multiplexor

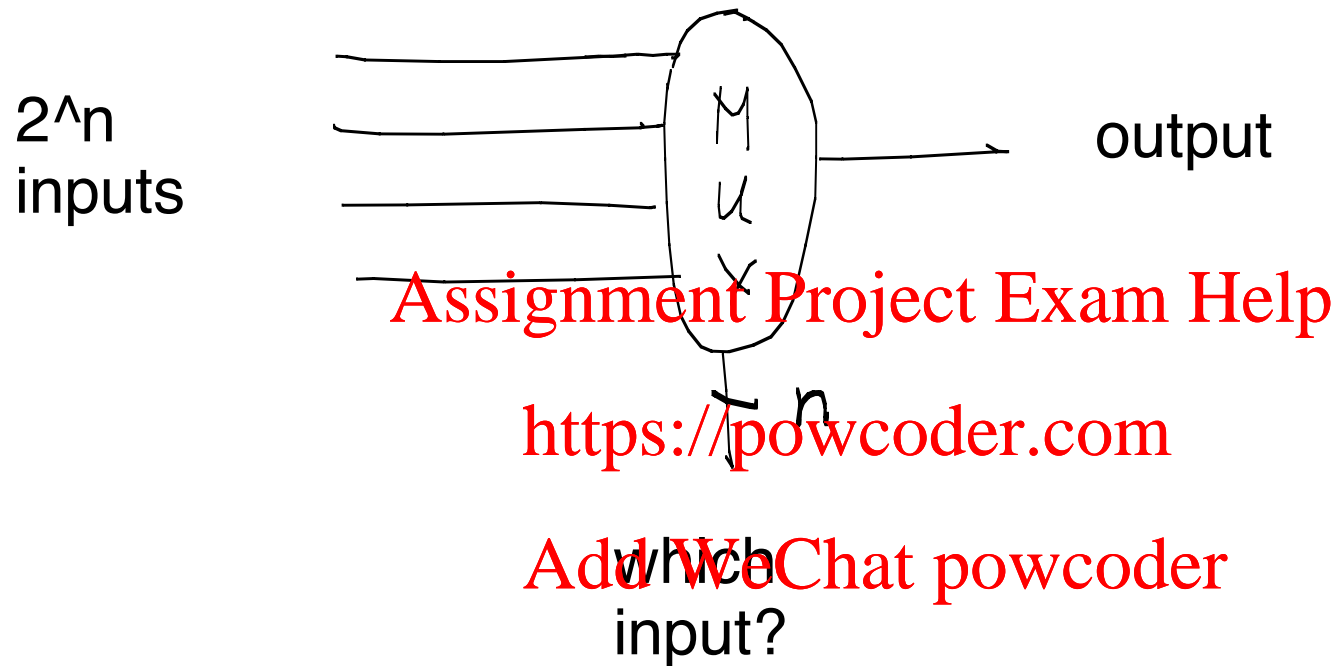

We will next look at some examples of how multiplexors are used.



Recall the ripple adder.

The main problem is that it is slow.


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

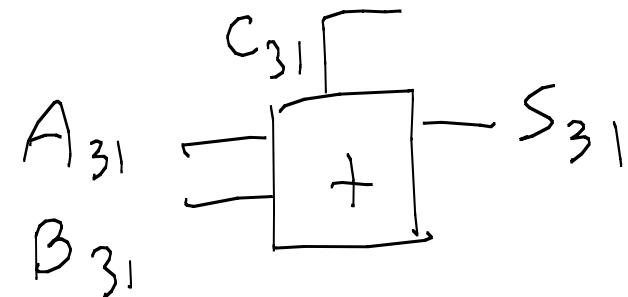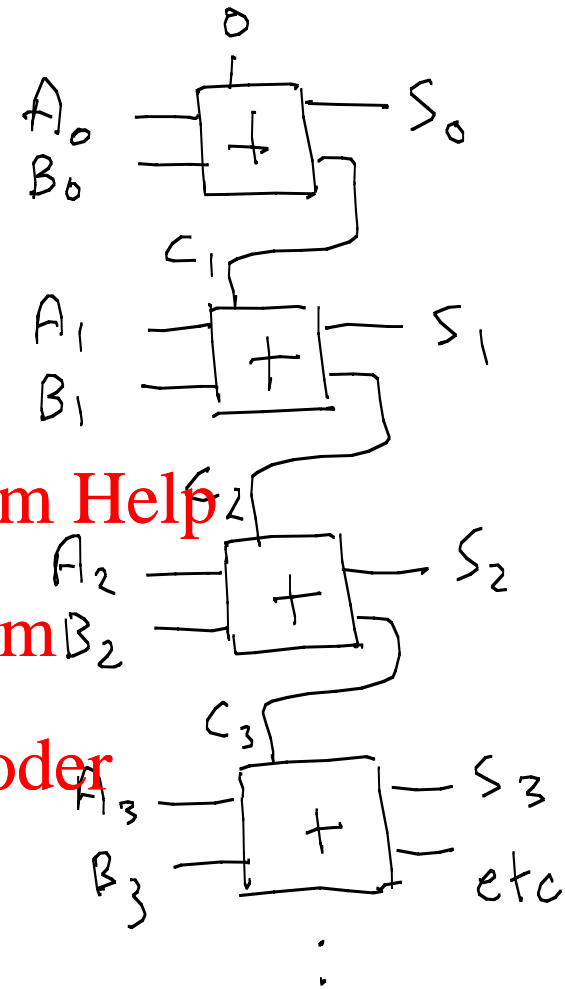


# How to speed up the adder ?

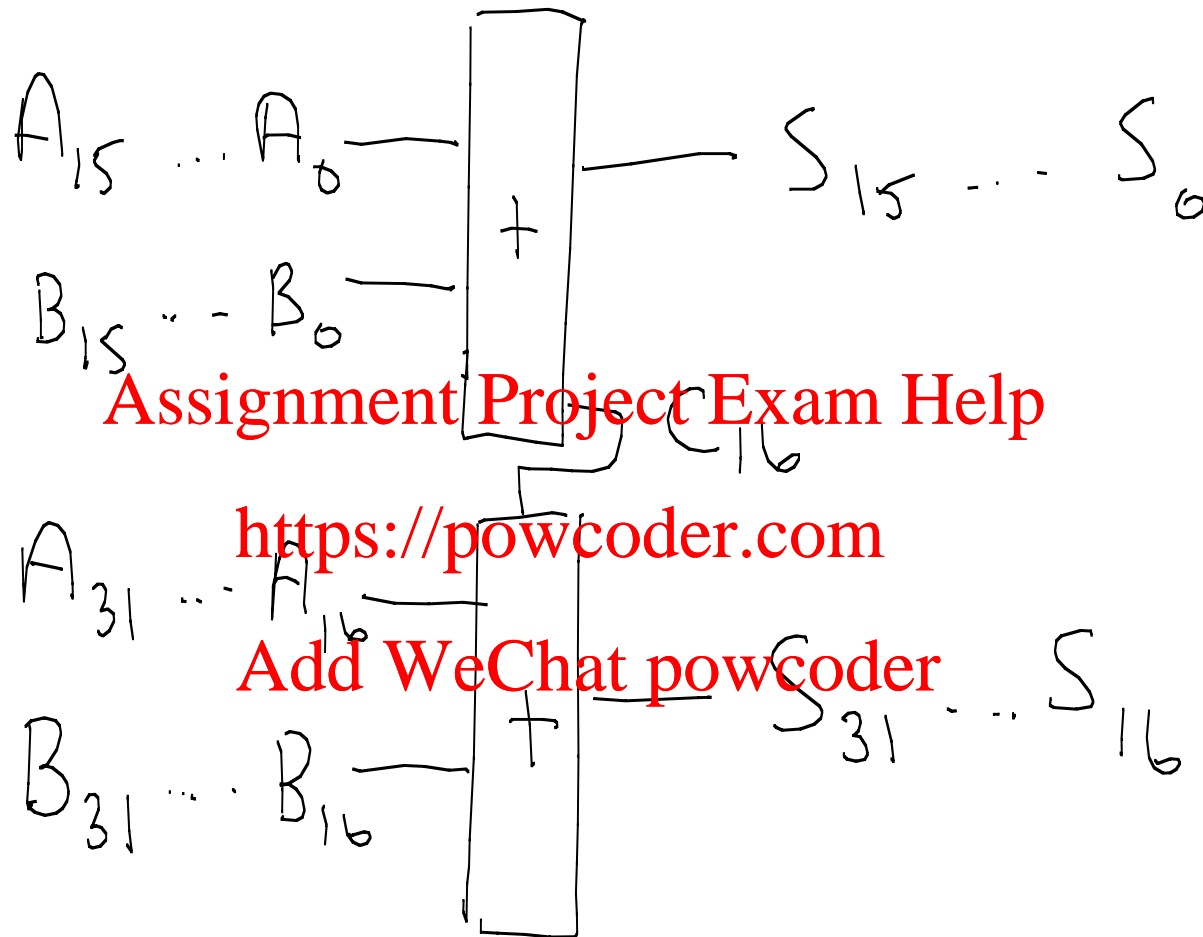

Instead of one 32 bit adder, think of two 16 bit adders.

We can compute the result of each, in half the time. (However, if  $C_{16} = 1$ , then we have to wait for it to ripple through. )

# Fast Adder

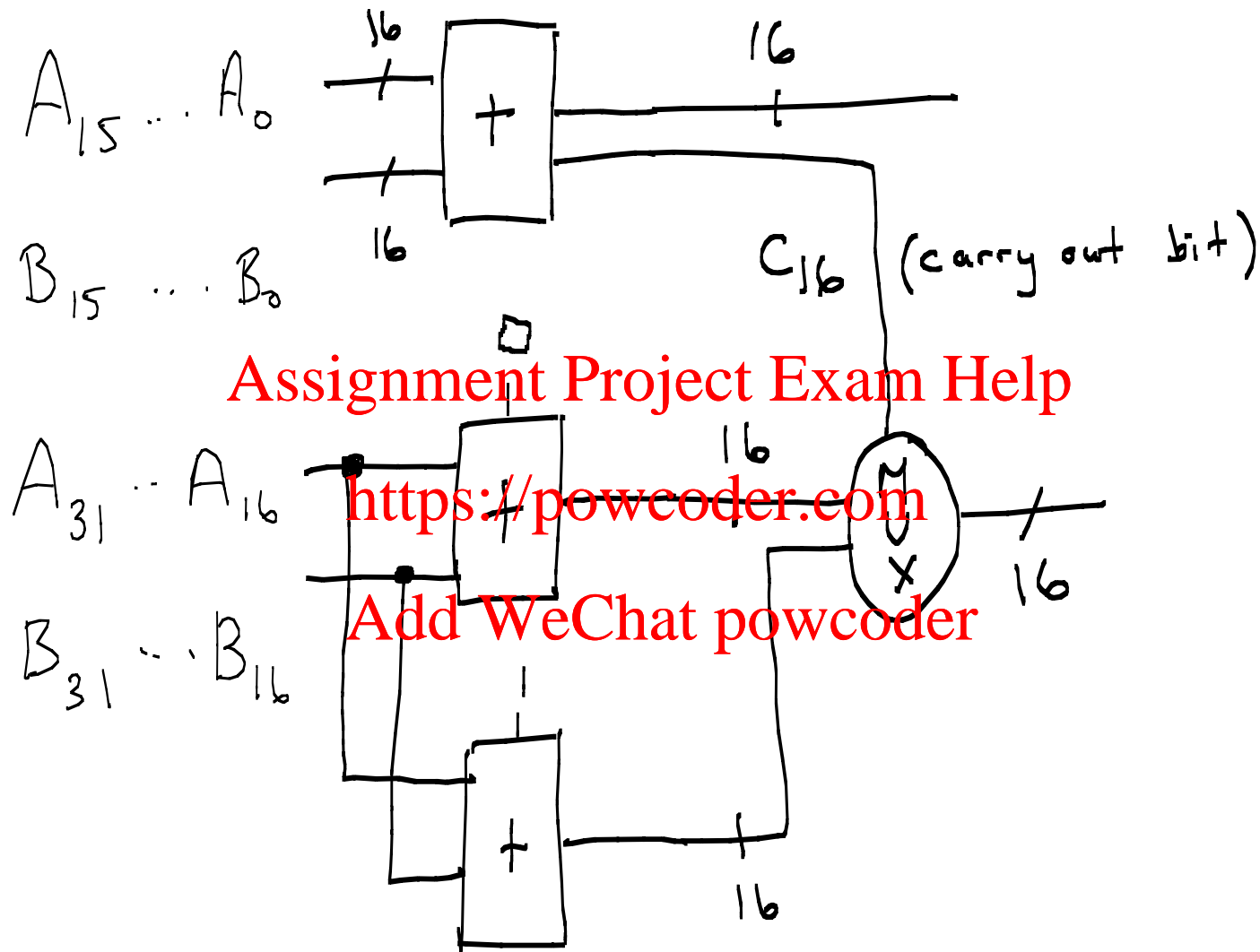

Tradeoffs: we chop the time in half (almost, why?) but it increases the number of gates by more than 50% (why?). Note we can repeat this idea (recursion).



# Subtraction

$$\begin{array}{r}
 A_{n-1} \dots A_2 A_1 A_0 \\
 - B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

$$x - y = x + (-y)$$

↑


Invert bits and add 1.

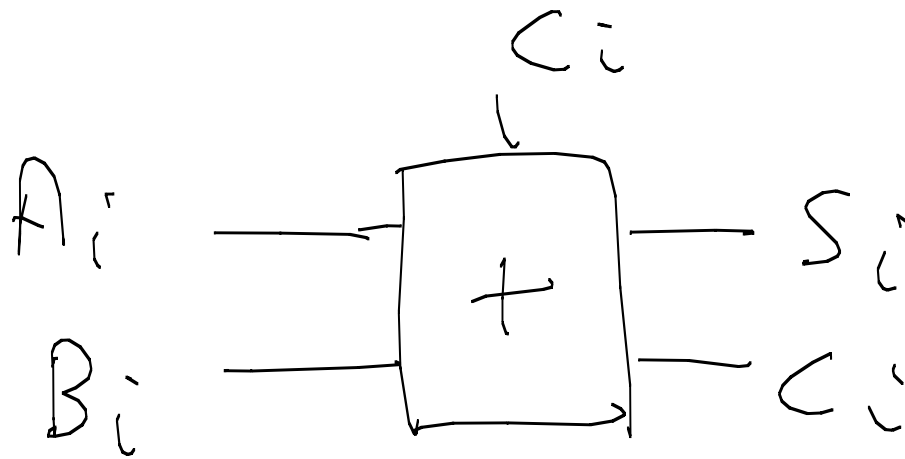

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

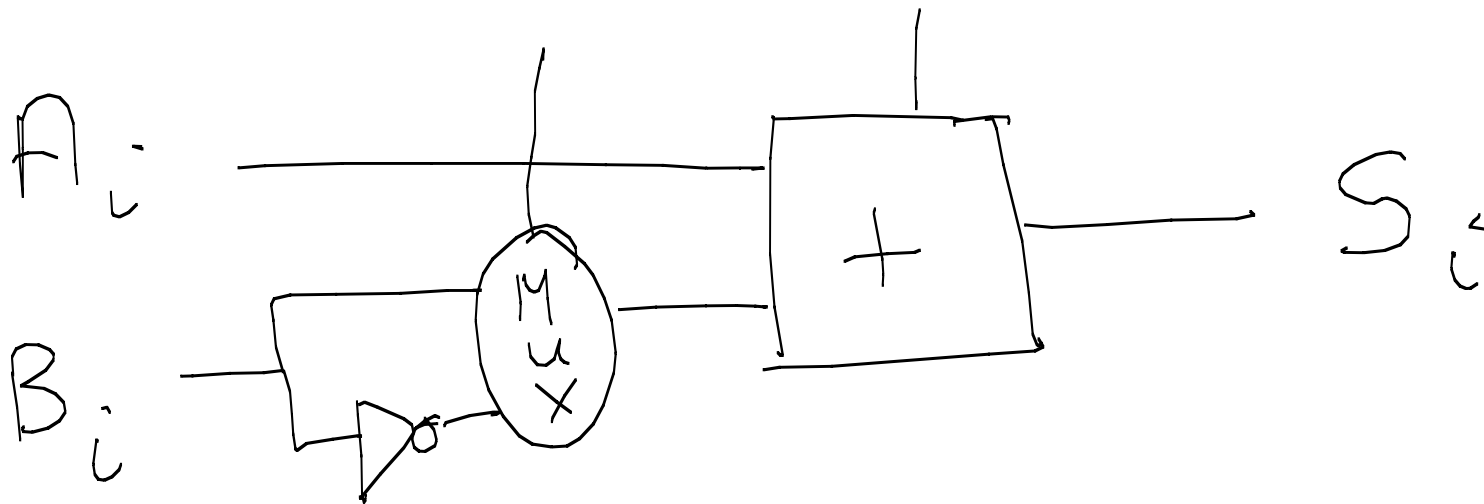

Invert bits and add 1.

When  $B_{\text{invert}}$  is 1, this adds 1 by setting  $C_0$  to 1.


(And also each bit in B is inverted)

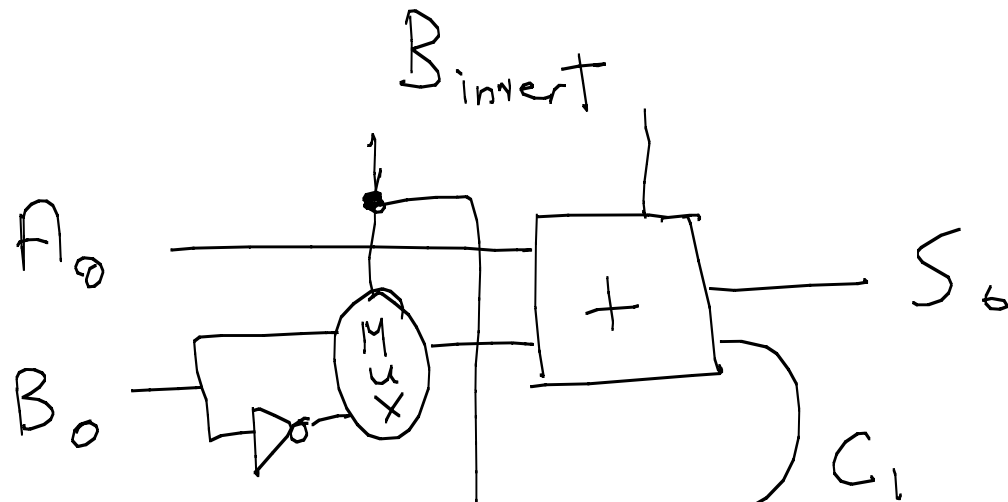

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

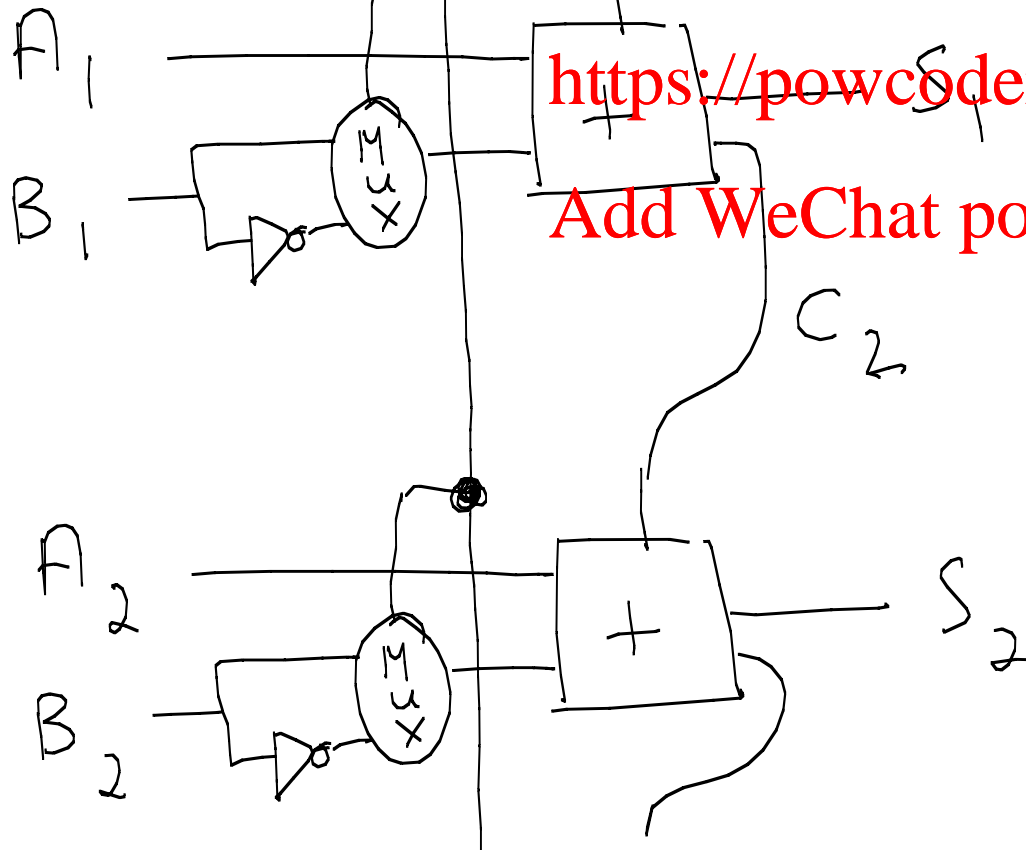

$$\begin{array}{r}
 A_{n-1} \dots A_2 A_1 A_0 \\
 B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

$n = 32$

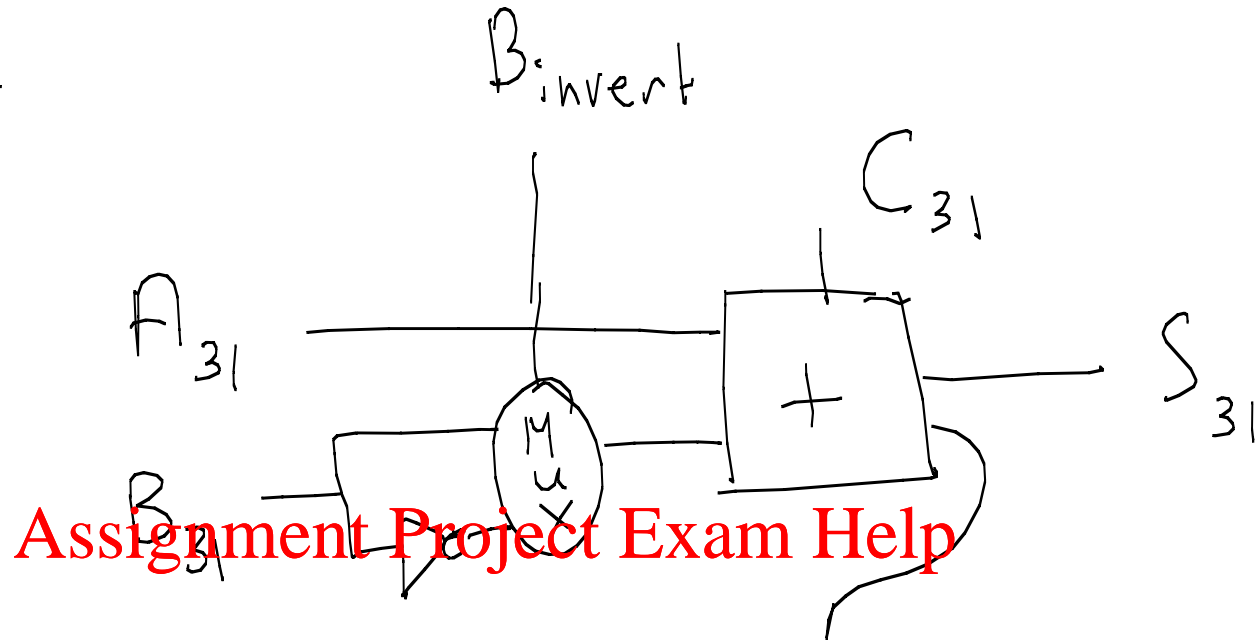

Assignment Project Exam Help

<https://powcoder.com>


overflow

Add WeChat powcoder

$B_{invert}$	$A_{31}$	$B_{31}$	$S_{31}$	overflow
0				
1				

See Exercises 2

# Let's include a bitwise AND and OR.

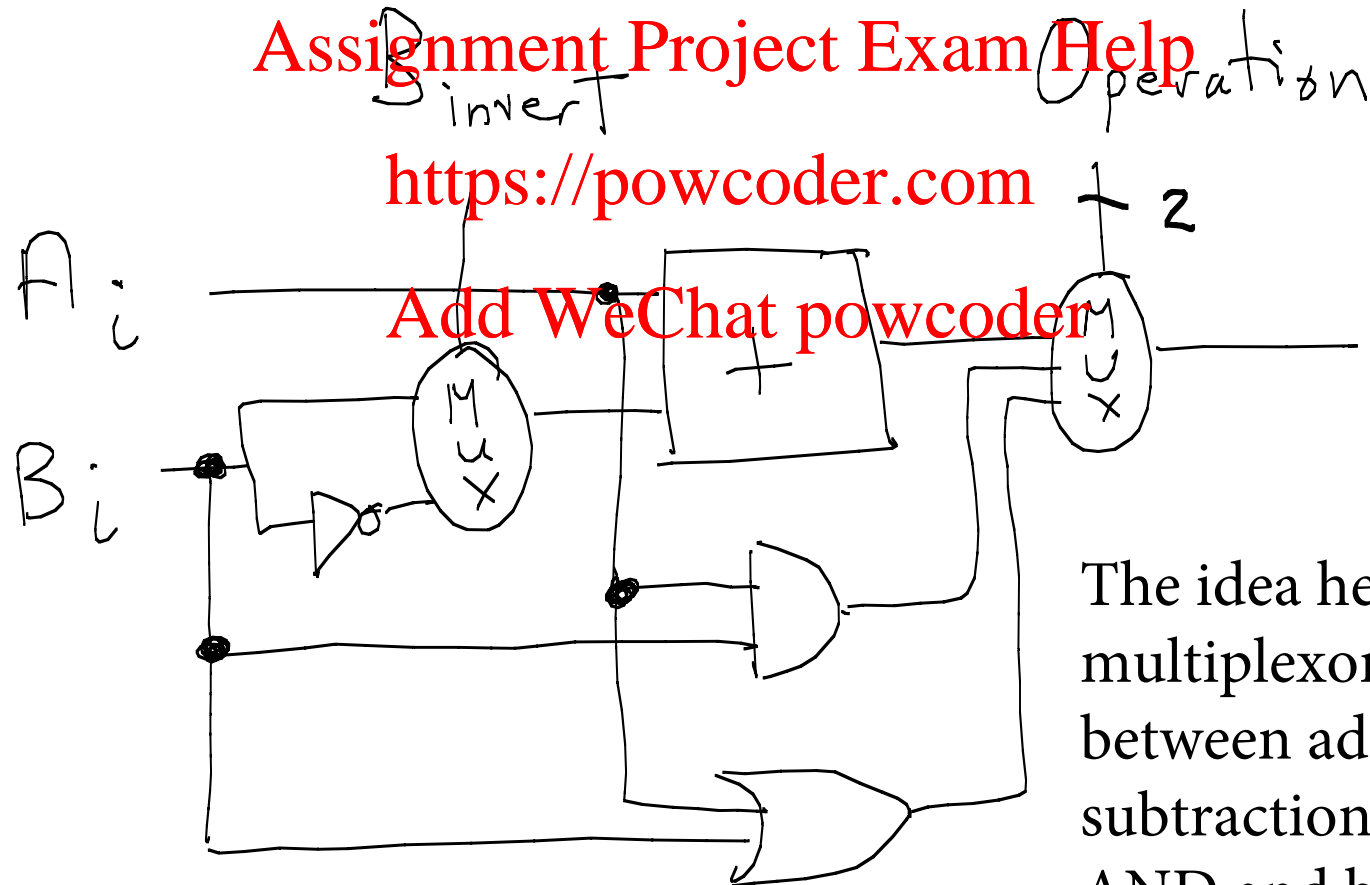

The idea here is that the multiplexor chooses between addition/subtraction, bit-wise AND and bit-wise OR.

# Arithmetic Logic Unit (ALU)

